

ELEC 2110

Electric Circuit Analysis

Gabriel Emerson

Jake Bryson

November 12, 2019

Section 002

Electrical Measurements: AC Power

Introduction

This lab will require the students to breadboard a variety of AC circuits using the NI ELVIS board, and a few basic components. Then the student will make a variety of measurements and then perform an array of calculations.

Exercise 1


Use your digital multimeter to measure the exact value of R.

Summary Table

R (330 Ohm)	327 Ohm
L (0.4 H)	0.405 H
C (10uF)	9.83 uF

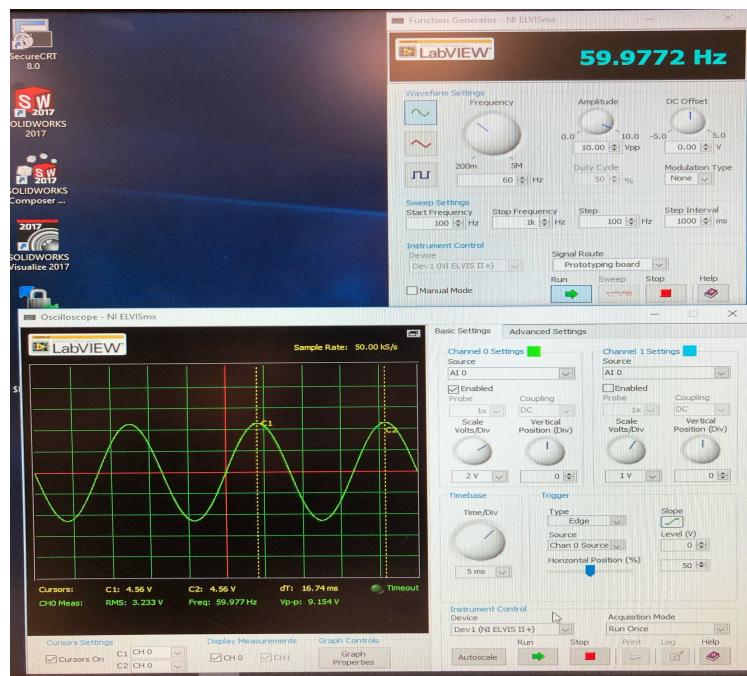Exercise 2

Setup Vs(t) using the function generator. Record the oscilloscope's measured value of the frequency and calculate the corresponding period, T(1/f).



(1)


FGEN and Oscilloscope for exercise 2

Summary Table

Frequency	= 59.977 Hz
Period = T(1/f)	= 16.75 Hz

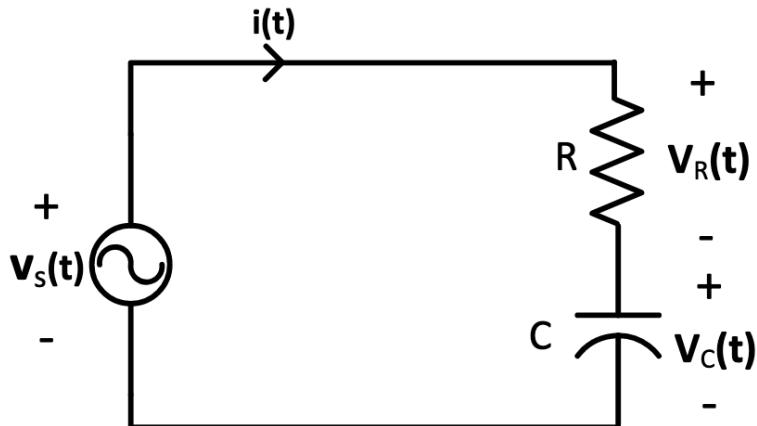
Exercise 3

Breadboard the circuit given. Then, use the scope to measure and record the RMS voltages. Then find the phase angles of R and C. Then find the following: Phase current, Phase difference between the capacitor voltage and current (is this value what you would expect and why), Complex power absorbed by the load S_{load} , Power factor of the load pF_{load} , Series reactance of the load X , the value of C.




(2)

Circuit given for exercise 3

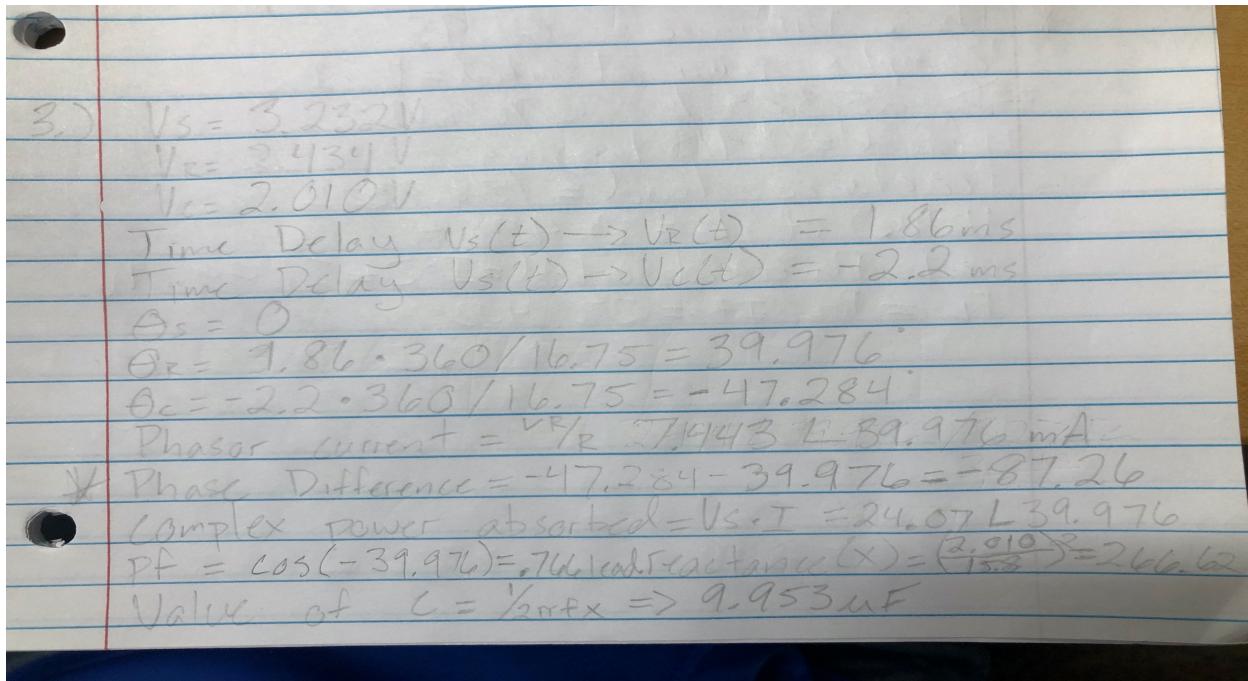


(3)

Equations for exercise 3

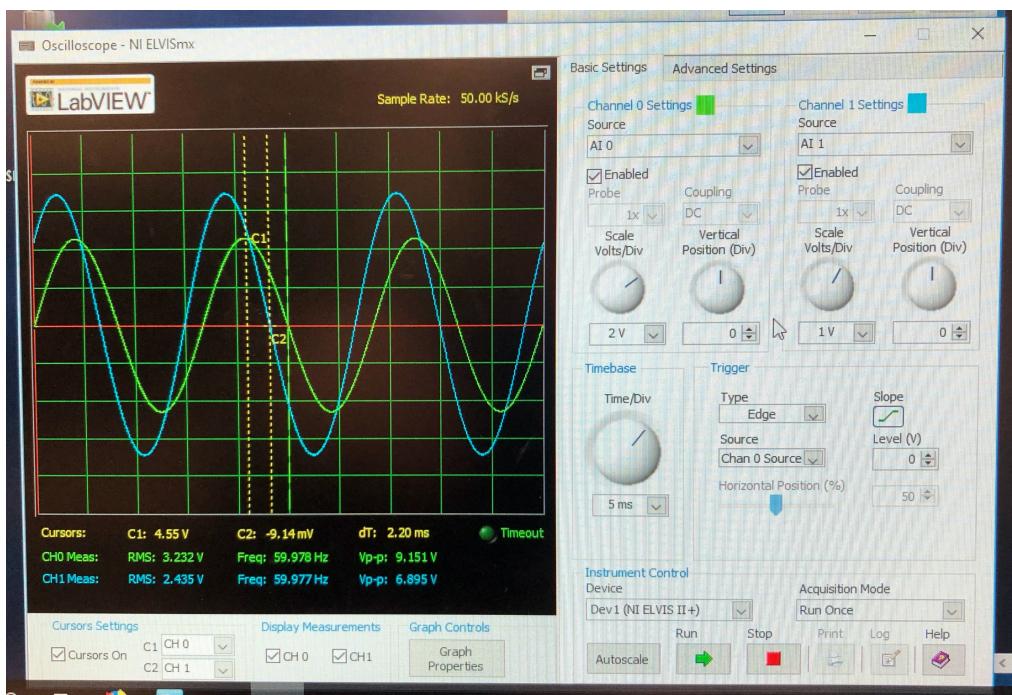

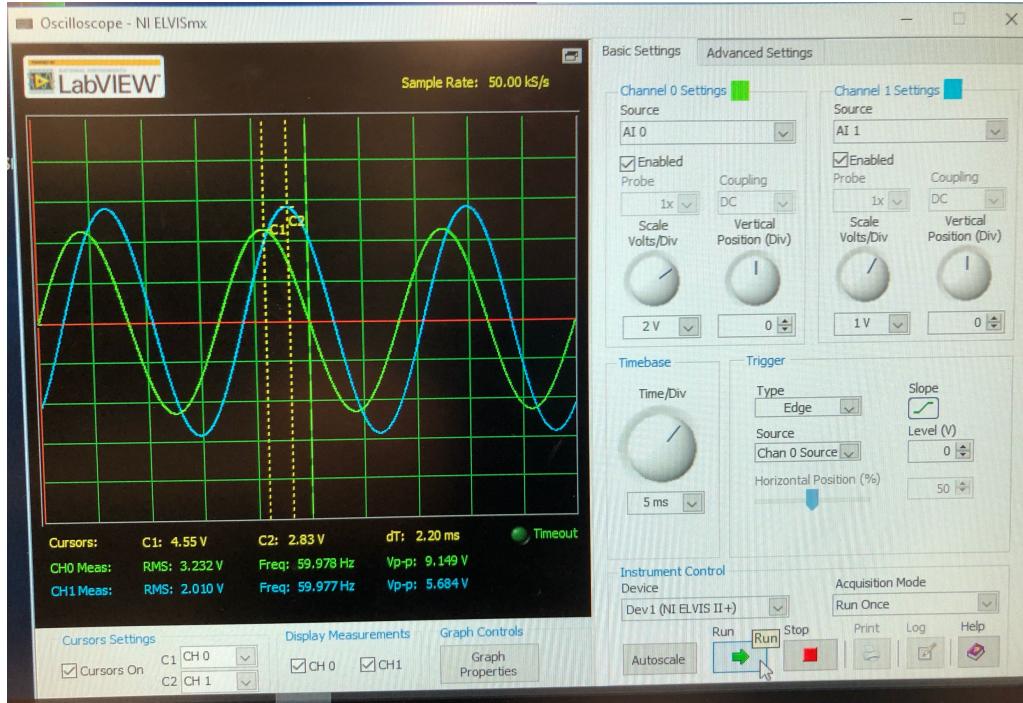(4)

Scope with time delay of $V_s(t)$ and $V_r(t)$



(5)


Scope with time delay of $V_s(t)$ and $V_c(t)$

Summary Table

Variable	Answer
V_s (RMS)	3.232 V
V_r (RMS)	2.434 V
V_c (RMS)	2.010 V
Time Delay (R)	1.86 ms
Time Delay (C)	-2.2 ms
Phase Angle (S) (In Degrees)	0
Phase Angle (R) (In Degrees)	39.976
Phase Angle (C) (In Degrees)	-47.284
Phasor Current (I)	$7.443 < 39.976$
Phase Difference	-87.26
Is this what is expected?	**Yes, capacitor voltage should lag current phase by 90 degrees.
Complex Power absorbed	$24.07 < 39.976$ mW
Power Factor of the load (pf_{load})	0.7661 leading
Series Reactance (X)	266.62 Ohm
Value of C	9.953 uF

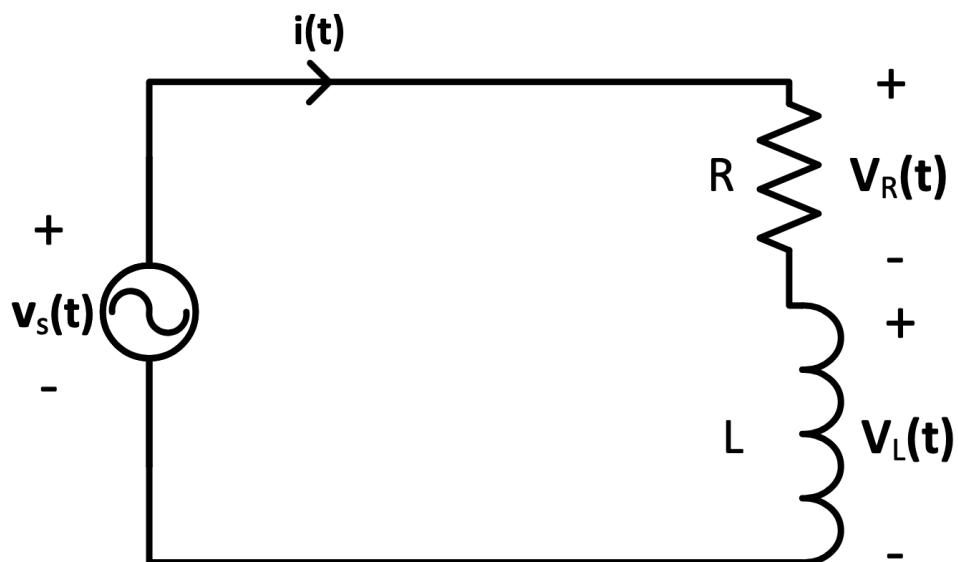Exercise 4

Breadboard the circuit given. Then, use the scope to measure and record the RMS voltages. Then find the phase angles of R and L. Then find the following: Phase current, Phase difference between the capacitor voltage and current (is this value what you would expect and why), Complex power absorbed by the load S_{load} , Power factor of the load pF_{load} , Series reactance of the load X , the value of L, the real power absorbed by the resistor, the value of the inductors equivalent series resistance (rL).



(6)

Circuit given for exercise 4

* Not quite 90° due to inductor's resistance

$$4.) \quad V_s = 3.151V$$

$$V_R = 2.655V$$

$$V_L = 1.271V$$

$$\text{Time Delay } V_s(t) + \tau V_R(t) = -1.1 \text{ ms}$$

$$\text{Time Delay } V_s(t) \rightarrow V_L(t) = 2.74 \text{ ms}$$

$$\theta_S = 0$$

$$\theta_R = -23.76$$

$$\theta_L = 59.17$$

$$\text{Phasor current} = 8.119 L - 23.76 \text{ mA}$$

$$* \text{Phase Difference} = 82.93^\circ$$

$$\text{Complex power absorbed} = V_s \cdot I$$

$$\Rightarrow 25.583 L - 23.76 \text{ mW}$$

$$\text{pf load} = 0.915 \text{ lagging}$$

$$\text{Reactance load} = 158.73 \Omega$$


$$\text{Value of } L = 10.421 \text{ H}$$

$$\text{real Power absorbed} = I^2 R = 21.99 \text{ mW}$$

$$r_L = P_R / I^2 = 27.64 \Omega$$


(7)

Equations for exercise 4

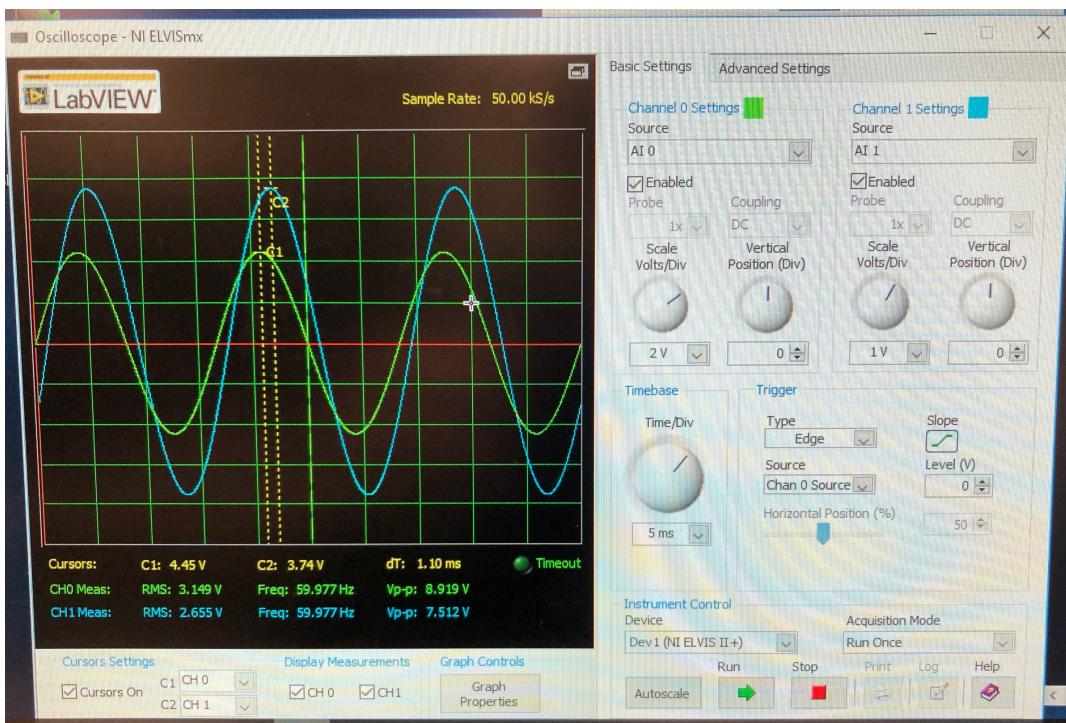

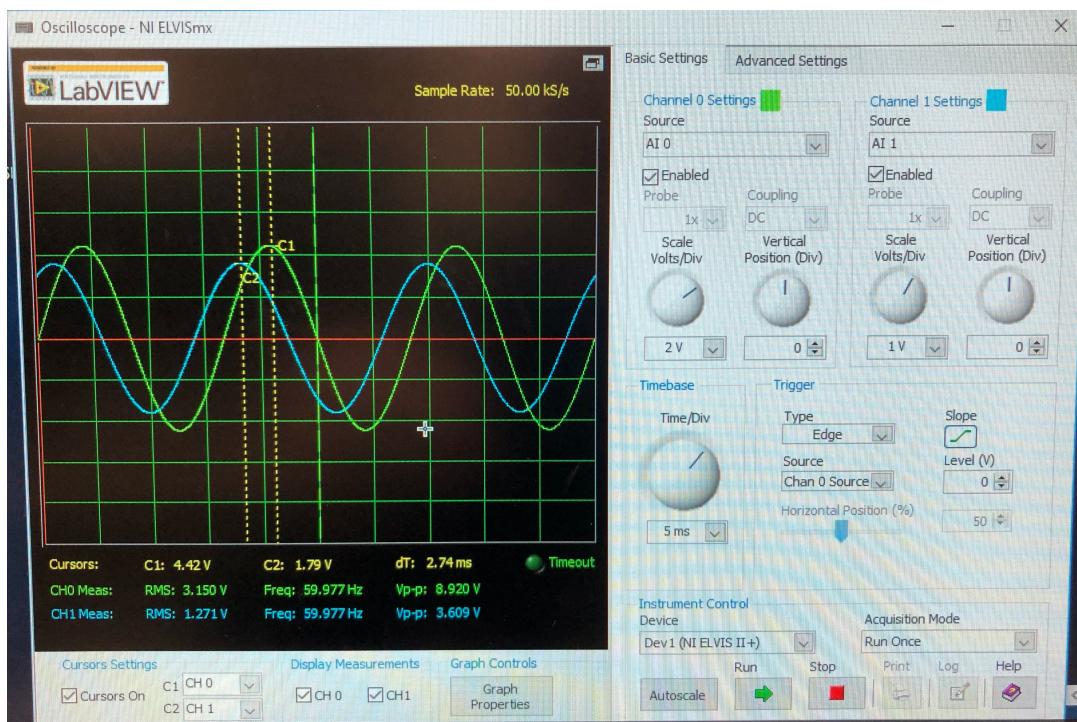(8)

Scope with time delay of $V_s(t)$ and $V_r(t)$



(9)


Scope with time delay of $V_s(t)$ and $V_l(t)$

Summary Table

Variable	Answer
V _s (RMS)	3.151 V
V _r (RMS)	2.655 V
V _l (RMS)	1.271 V
Time Delay (R)	-1.11 ms
Time Delay (L)	2.74 ms
Phase Angle (S) (In Degrees)	0
Phase Angle (R) (In Degrees)	-23.76
Phase Angle (L) (In Degrees)	59.17
Phasor Current (I)	8.119 <-23.76
Phase Difference **Is this what is expected?**	82.93 **Not quite 90 degrees due to inductors resistance.
Complex Power absorbed	25.583 <-23.76 mW
Power Factor of the load (pf_load)	0.915 lagging
Series Reactance (X)	158.73 Ohm
Value of L	0.421 H
Real Power absorbed	21.99 mW
rL	27.64 Ohm

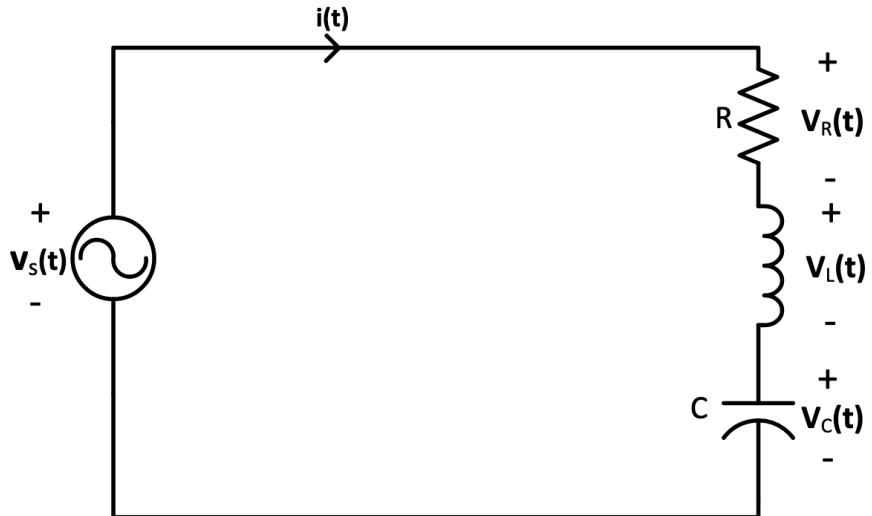Exercise 5

Breadboard the circuit given. Then, use the scope to measure and record the RMS voltages. Then find the phase angles of R, L, and C. Then find the following: Phase current, Complex power absorbed by the load S_load, Power factor of the load pF_load, Complex Power absorbed individually by R, L, and C (and confirm they equal total real power absorbed), the equivalent series load impedance Z. Also write the full expressions for V_s(t), V_r(t), V_l(t), V_c(t), and i(t).



(10)


Circuit given for exercise 5

$v_s = 3.148 \text{ V}$ $v_R = 2.576 \text{ V}$ $v_L = 1.269 \text{ V}$ $v_C = 2.188 \text{ V}$ Time Delay: $v_s(t) \rightarrow v_R(t) = 0.88 \text{ ms}$ $v_s(t) \rightarrow v_L(t) = 4.74 \text{ ms}$ $v_s(t) \rightarrow v_C(t) = -3.2 \text{ ms}$	Write Full Expressions For: $v_s(t) = 4.436 \cos(377t + 0^\circ) \text{ V}$ $v_R(t) = 3.755 \cos(377t + 19^\circ) \text{ V}$ $v_L(t) = 1.827 \cos(377t + 102.4^\circ) \text{ V}$ $v_C(t) = 3.199 \cos(377t - 169.12^\circ) \text{ V}$ $i(t) = 11.74 \cos(377t + 19^\circ) \text{ mA}$
--	--

Phaser Current = $8.30 \angle -19.3 \text{ mA}$
 Complex Power absorbed = $26.04 \angle -19.0 \text{ mVA}$
 PF load = 0.945 leading
 Complex Power absorbed individually:
 $R = 22.04 + j0 \text{ mVA}$
 $L = 1.23 + j10.65 \text{ mVA}$
 $C = 0.6 - j18.76 \text{ mVA}$
 $\therefore \text{Impedance } Z = 357.8 - j123.2$


(11)

Equations for exercise 5

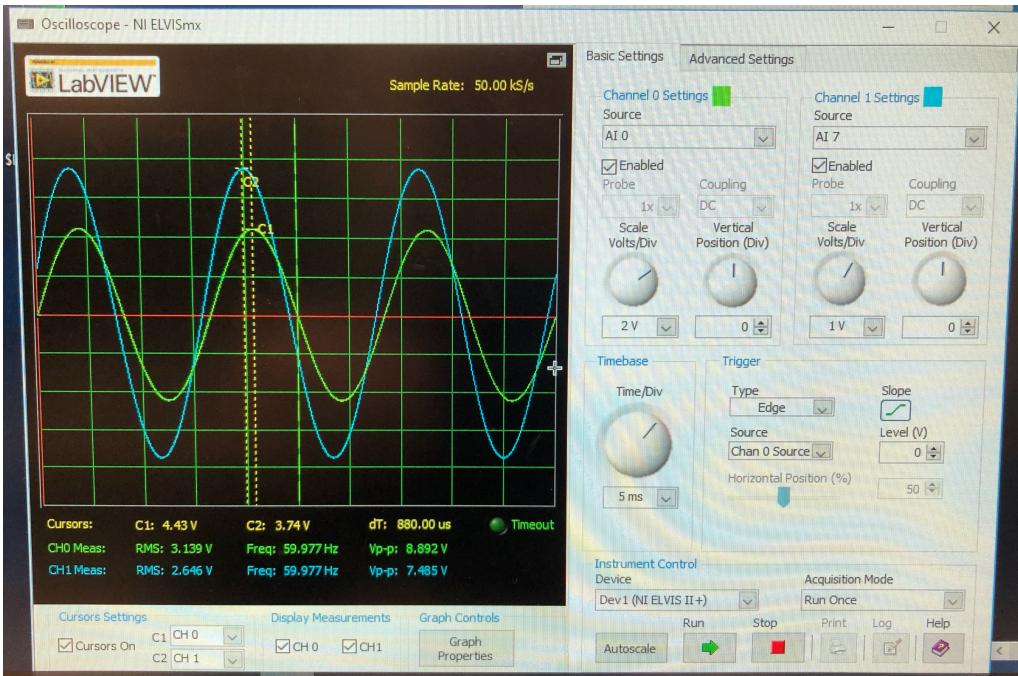

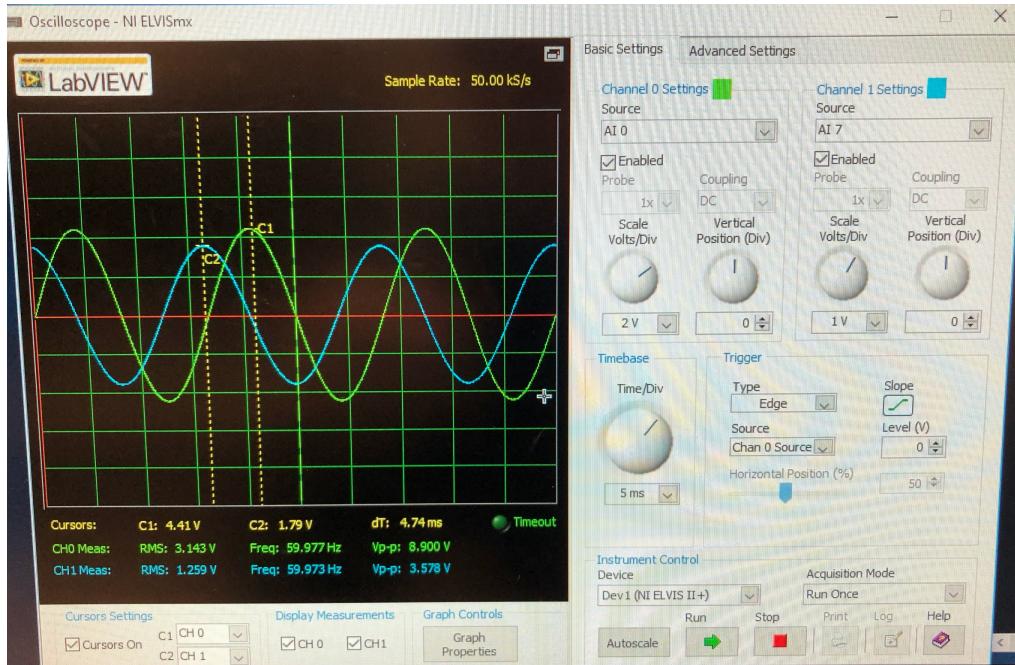
(12)

Scope with time delay of $V_s(t)$ and $V_r(t)$



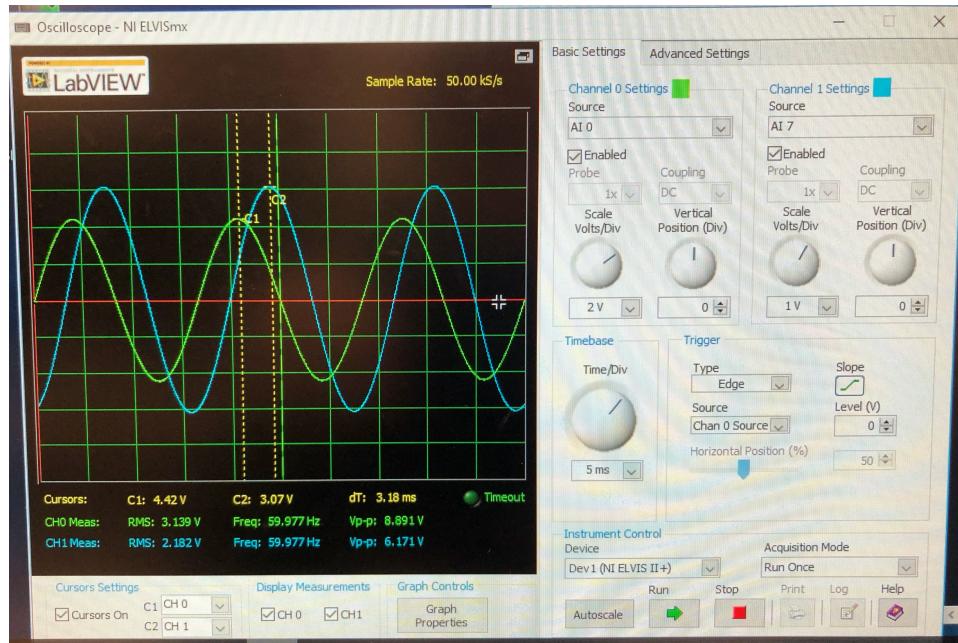(13)

Scope with time delay of $V_s(t)$ and $V_l(t)$



(14)

Scope with time delay of $V_s(t)$ and $V_c(t)$

Summary Table

V_s (RMS)	3.148 V
V_r (RMS)	2.574 V
V_l (RMS)	1.269 V
V_c (RMS)	2.188 V
Time Delay $V_s(t) \rightarrow V_r(t)$	0.88 ms
Time Delay $V_s(t) \rightarrow V_l(t)$	4.74 ms
Time Delay $V_s(t) \rightarrow V_c(t)$	-3.20 ms
Phase Angle (S) (Degrees)	0
Phase Angle (R) (Degrees)	19.0
Phase Angle (L) (Degrees)	102.4
Phase Angle (C) (Degrees)	-69.12
Phasor Current	$8.30 < 19.0$ mA
Complex Power Absorbed	$26.04 < -19.0$ mVA
pF load	0.945 leading
Complex power absorbed individual:	
1. Resistor (R)	$1. 22.04 < 0$ mVA
2. Inductor (L)	$2. 10.721 < 83.4119$ mVA
3. Capacitor (C)	$3. 18.7696 < -88.1681$ mVA
Impedance (Z)	$378.417 < -18.999$ Ohm

Write Full Expressions for:

$$V_s(t) = 4.436 \cos(377t+0) \text{ V}$$

$$V_r(t) = 3.755 \cos(377t+19) \text{ V}$$


$$V_l(t) = 1.827 \cos(377t+102.4) \text{ V}$$

$$V_c(t) = 3.199 \cos(377t-69.12) \text{ V}$$

$$i(t) = 11.74 \cos(377t+19) \text{ mA}$$

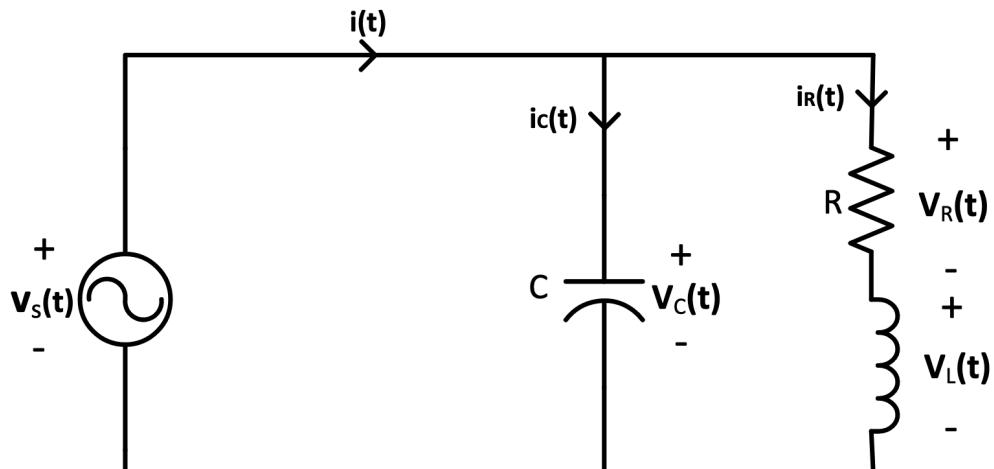Exercise 6

Breadboard the circuit given. Then, use the scope to measure and record the RMS voltages. Then find the phase angles of R, L, and C. Then find the following: Phase currents (i_R and i_C), Complex power absorbed by the C branch and by the R-L branch, Complex total power absorbed S_{load} , Power factor of the load pf_{load} (**To obtain a unity power factor ($\text{pf}_{\text{Load}} = 1$), should the parallel capacitor be increased or decreased**), the equivalent series load impedance Z .



(15)

Circuit given for exercise 6

$$Z_C = \frac{-j}{2\pi(59.98)(10)} \Rightarrow -j26.39\Omega$$

6.) $V_S = 3.099V$

$$V_R = 2.619V$$

$$V_L = 1.249V$$

Time Delays:

$$V_S(t) \rightarrow V_R(t) = -1.1ms$$

$$V_S(t) \rightarrow V_C(t) = 0ms$$

$$V_S(t) \rightarrow V_L(t) = 2.64ms$$

$$\theta_S = 0^\circ$$

$$\theta_R = -23.76^\circ$$

$$\theta_C = 0^\circ$$

$$\theta_L = 57.01^\circ$$

Phasor Current:

$$I_R = 11.71 L 90^\circ$$

$$I_C = 8.18 L -23.76^\circ$$

$$S_C = 0 - j34.34 \text{ mVA}$$

$$S_{RL} = 23.27 + j10.24 \text{ mVA}$$

$$\text{Phasor Current} = 11.26 L 48.34 \text{ mA}$$

$$S_{\text{load}} = 23.3 - j26.15 \rightarrow 35 L - 48.34 \text{ mVA}$$

$$\text{PF}_{\text{load}} = \cos(-48.34) = 0.66417 \text{ leading}$$

* A smaller capacitor would be needed


* Since PT was lagging with only R-L

$$\text{Impedance } (7) \frac{V_S}{I}$$

$$\Rightarrow 183.5 - j206.2 \rightarrow 276 L - 48.3$$


(16)

Equations for exercise 6

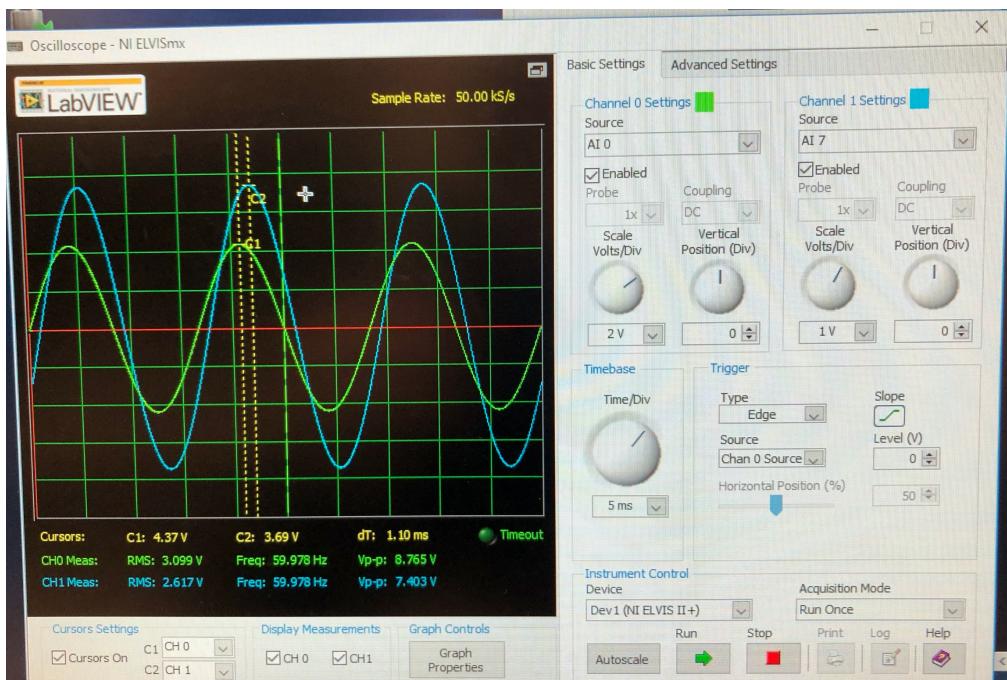

(17)

Scope with time delay of Vs(t) and Vr(t)

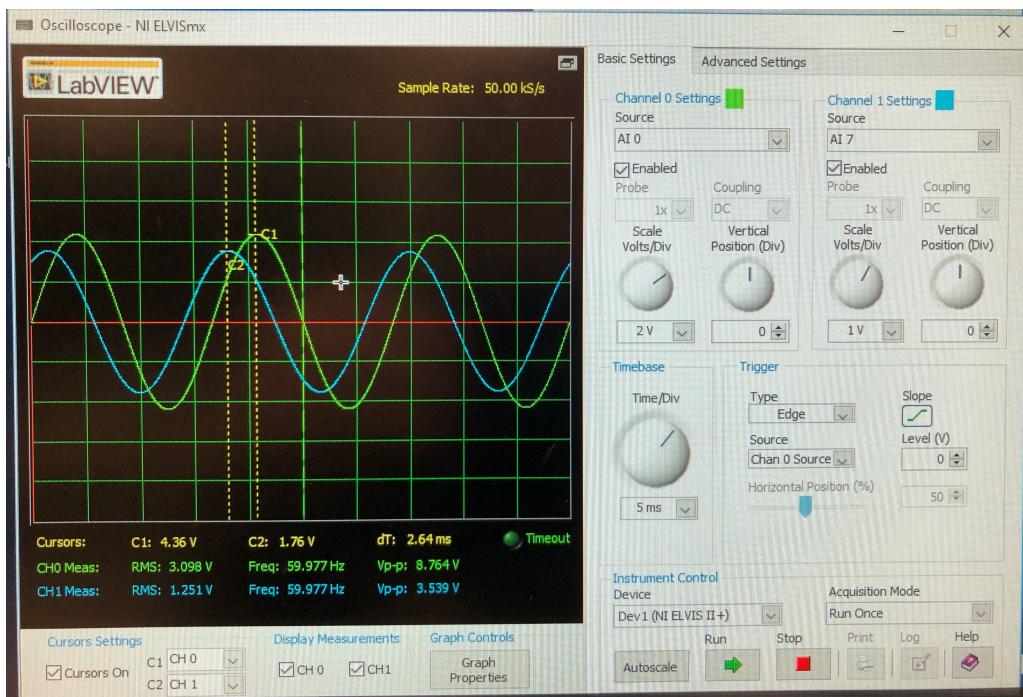

(18)

Scope with time delay of Vs(t) and Vl(t)

Summary Table

Vs (RMS)	3.099 V
Vr (RMS)	2.619 V
Vl (RMS)	1.249 V
Time Delay Vs(t)→Vr(t)	-1.10 ms
Time Delay Vs(t)→Vl(t)	2.64 ms
Time Delay Vs(t)→Vc(t)	0 ms
Phase Angle (S) (Degrees)	0
Phase Angle (R) (Degrees)	-23.76
Phase Angle (L) (Degrees)	57.01
Phase Angle (C) (Degrees)	0
Phasor Current (Ir)	11.71 <90
Phasor Current (Ic)	8.18 <-23.76
Complex Power Absorbed:	
1. C-branch	1. 36.36 <-90 mVA
2. R-L branch	2. 25.4234 <23.752
3. Total (S_load)	3. 34.9821 <-48.3025
pF_load ** To obtain a unity power factor (pF_Load = 1), should the parallel capacitor be increased or decreased?**	0.6647 leading **A smaller capacitor would be needed since pF was lagging with only R-L in the circuit**
Impedence (Z)	276 <-48.3 Ohm

Conclusion

This lab is quite important since it gives real-world scenarios to the student to solve. Since we have studied all of circuit engineering, we have moved past that and are now studying power lines and how AC circuits affect the real world. The knowledge of power and how to calculate certain parts of it, is very important to an electrical engineer since it is one of the main routes an electrical engineer can go.

Bibliography

1. FGEN and Oscilloscope for exercise 2
2. Circuit given for exercise 3
3. Equations for exercise 3
4. Oscilloscope with time delay for $V_s(t)$ to $V_r(t)$
5. Oscilloscope with time delay for $V_s(t)$ to $V_c(t)$
6. Circuit given for exercise 4
7. Equations for exercise 4
8. Oscilloscope with time delay for $V_s(t)$ to $V_r(t)$
9. Oscilloscope with time delay for $V_s(t)$ to $V_l(t)$
10. Circuit given for exercise 5
11. Equations for exercise 5
12. Oscilloscope with time delay for $V_s(t)$ to $V_r(t)$
13. Oscilloscope with time delay for $V_s(t)$ to $V_l(t)$
14. Oscilloscope with time delay for $V_s(t)$ to $V_c(t)$
15. Circuit given for exercise 6
16. Equations for exercise 6
17. Oscilloscope with time delay for $V_s(t)$ to $V_r(t)$
18. Oscilloscope with time delay for $V_s(t)$ to $V_l(t)$