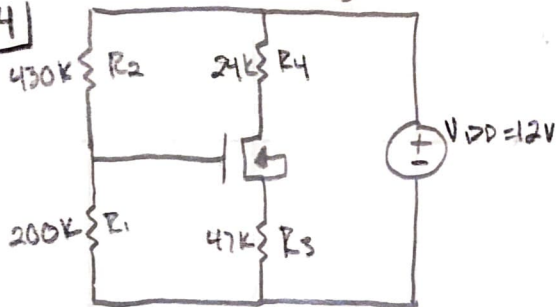


Gabriel Emerson gte0002 4R Bias HW1 Due 3/28

4.94



$$V_{TO} = 1V$$

$$\gamma = 0$$

$$\frac{W}{L} = \frac{5}{1}$$

$$K_{Pn} = 100 \frac{\mu A}{V^2}$$

$$K_{Pp} = 40 \frac{\mu A}{V^2}$$

Assume sat: $I_{DS} = \frac{1}{2} K V_{GS}^2$, $K = K_{Pn} \cdot \frac{W}{L}$

$$V_{GS} = \frac{V_{DD}}{R_1 + R_2} \cdot R_1 = \frac{12}{200k + 430k} \cdot 200k = 3.81V$$

$$V_{GS} = V_{GS} + V_{TN}$$

$$V_{GS} = V_{GS} + V_{TN} + V_S \Rightarrow 3.81 = V_{GS} + V_{TN} + \frac{K_n}{2} V_{GS}^2 \cdot R_S$$

$$\frac{K_{Pn} \cdot R_S}{2} \cdot V_{GS}^2 + V_{GS} - 2.81 = 0$$

$$\frac{K_{Pn} \cdot R_S}{2} = \frac{100 \mu A \cdot 5 \cdot 47k}{2}$$

$$= 11.75$$

$$11.75 V_{GS}^2 + V_{GS} - 2.81 = 0$$

$$\frac{-1 + \sqrt{1^2 - 4(11.75)(-2.81)}}{2(11.75)} = 0.448V = V_{GS}$$

$$I_{DS} = \frac{1}{2} K_{Pn} \frac{W}{L} \cdot V_{GS}^2 = 50 \mu A$$

$$V_{GS} = V_{GS} + V_{TN} = 1.448V$$

$$V_{DS} = V_{DD} - I_{DS}(R_S + R_D) = 12 - 50 \mu A (47k + 24k) = 8.45V$$

$$V_{DS} > V_{GS} \text{ Sat} \checkmark$$

$$Q_{point} = V_{GS} = 1.448V \quad I_{DS} = 50 \mu A \\ V_{DS} = 8.45V$$

$$2.) I_{DS} = 2\text{mA}$$

$$V_S = 3\text{V}$$


$$R_{eq} = 110\text{k}\Omega$$

$$V_{DD} = 15\text{V}$$

$$V_{GS} = 1.97 \text{ (from sim)}$$

$$V_G - V_S = 1.97$$

$$V_G = 1.97 + 3 = 4.97\text{V}$$

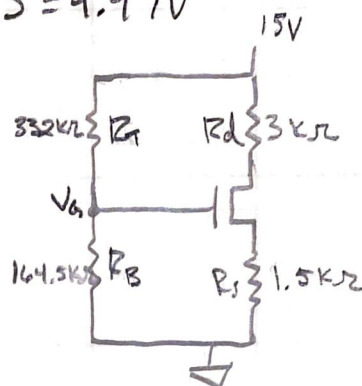

$$R_S = \frac{V_S}{I_{DS}} = \frac{3\text{V}}{2\text{mA}} = 1.5\text{k}\Omega$$

$$V_{Dl} = \frac{V_{DD} - V_S}{2} = \frac{15 - 3}{2} = 6\text{V}$$

$$R_{Dl} = \frac{V_{Dl}}{I_{DS}} = \frac{6\text{V}}{2\text{mA}} = 3\text{k}\Omega$$

$$V_{G1} = \frac{V_{DD}}{R_b + R_t} \cdot R_b \rightarrow V_{G1} \cdot R_t = R_{eq} \cdot V_{DD}$$

$$R_t = \frac{R_{eq} V_{DD}}{V_{G1}} = \frac{110\text{k}(15)}{4.97} = 331.992\text{k}\Omega = 332\text{k}\Omega$$

$$R_{eq} = \frac{R_t R_b}{R_t + R_b} \rightarrow R_{eq}(R_t + R_b) = R_t R_b$$

$$R_{eq} R_t + R_{eq} R_b = R_t R_b$$

$$R_b(R_t - R_{eq}) = R_{eq} R_t$$

$$R_b = \frac{R_{eq} R_t}{R_t - R_{eq}} = 164.51\text{k}\Omega$$

$$I_{DS\text{MAX}} = \frac{V_{DD} - V_S}{R_{Dl}} = \frac{15 - 3}{3\text{k}} = 4\text{mA}$$


$$I_{DS\text{min}} = \frac{5.05 - 3}{3\text{k}} = 0.68\text{mA} \text{ when on}$$

$$0\text{mA} \text{ when off}$$

```

.param Vdd=12
.model NMOS NMOS(KP=100u VTO=1)
.op


```

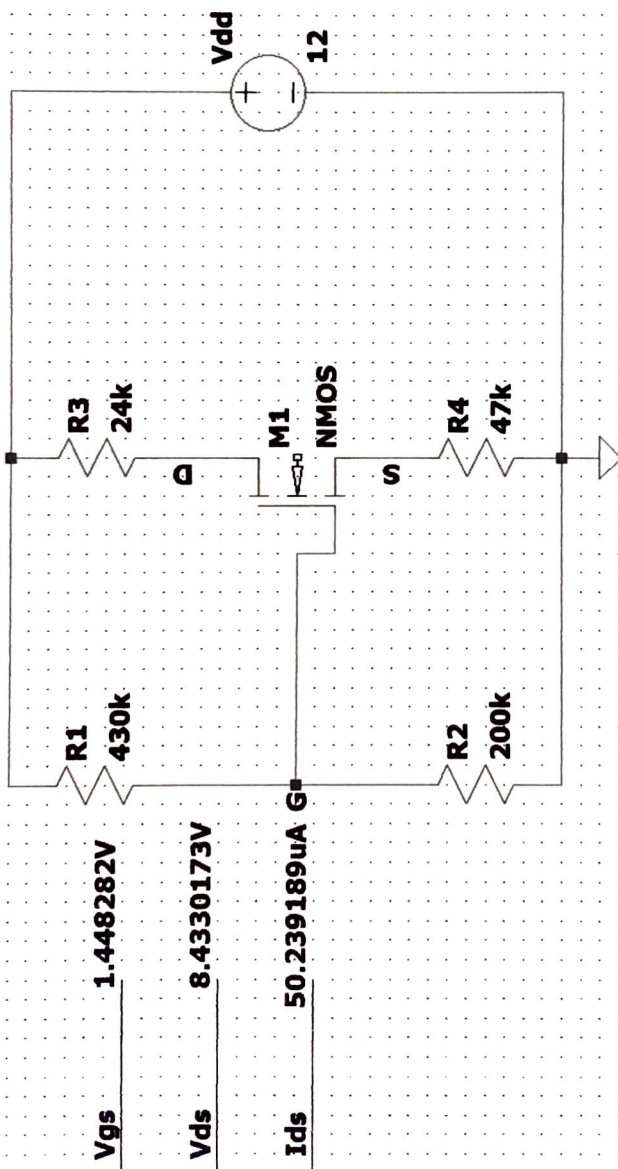

C:\Users\bobog\Desktop\School\Digital Electronics\Home...

--- Operating Point ---

Variable	Value	Unit	Device
V(d)	10.7943	voltage	
V(g)	3.80952	voltage	
V(s)	2.36124	voltage	
V(m01)	2.52493	voltage	
V(m01)	12	voltage	
I(d(m1))	5.02392e-005	device_current	
I(g(m1))	0	device_current	
I(s(m1))	-2.52226e-012	device_current	
I(s(m1))	-5.02392e-005	device_current	
I(R4)	5.02392e-005	device_current	
I(R3)	5.02392e-005	device_current	
I(R2)	1.90476e-005	device_current	
I(R1)	1.90476e-005	device_current	
I(Vdd)	-6.92868e-005	device_current	

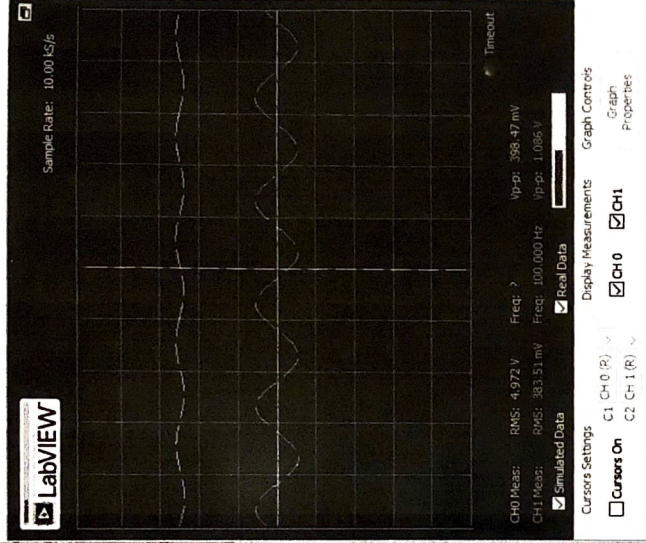

Basic Settings


Channel 0 Settings
Source: SCOPE CH 0
Probe: ☒ Enabled
Coupling: DC
Scale: 1 V/Div
Vertical Position (Div): 0
Timebase: 5 ms
Time/Div: 5 ms
Trigger: Type: Immediate, Source: Source, Horizontal Position (%): 50

Advanced Settings



Channel 1 Settings
Source: SCOPE CH 1
Probe: ☒ Enabled
Coupling: DC
Scale: 1 V/Div
Vertical Position (Div): 0
Timebase: 5 ms
Time/Div: 5 ms
Trigger: Type: Immediate, Source: Source, Horizontal Position (%): 50

Instrument Control

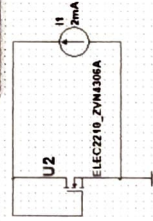Device: Simulate NI ELVIS II
Acquisition Mode: Run Continuously
Run: Run, Stop, Print, Log, Autoscale



ELEC2210_ZYM4306A

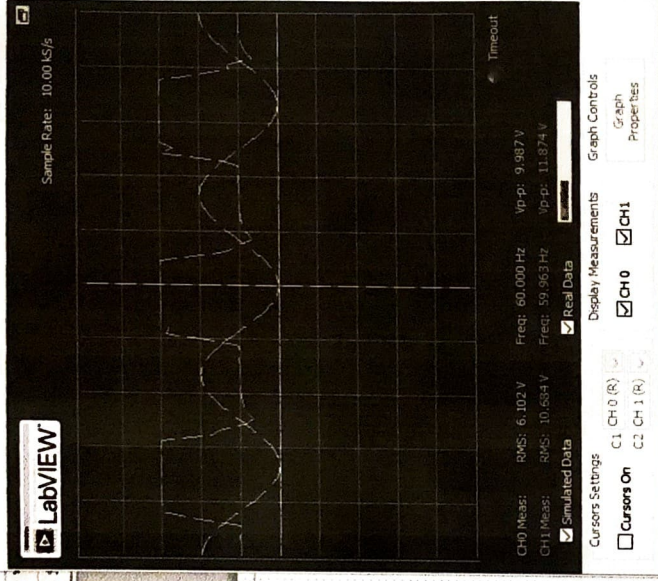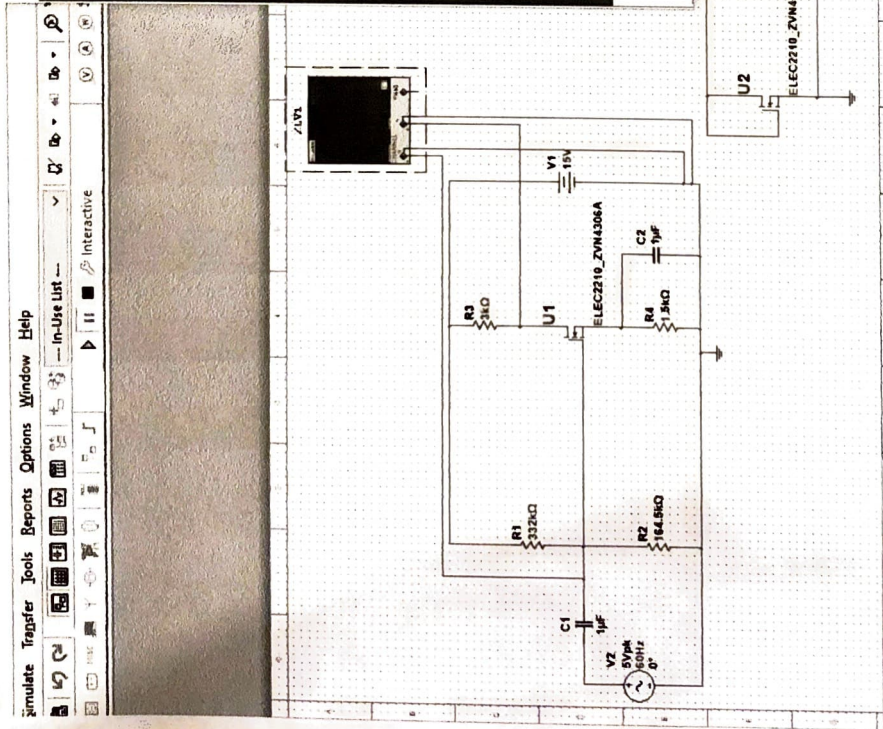

Basic Settings

Channel 0 Settings

Source

SCOPE CH 0

Enabled

Coupling

DC

Scale

Volts/Div

Vertical Position (Div)

5 V

0

Timebase

Time/Div

5 ms

Trigger

Type

Immediate

Source

Slope

Level (V)

0

Horizontal Position (%)

50

Advanced Settings

Channel 1 Settings

Source

SCOPE CH 1

Enabled

Coupling

DC

Scale

Volts/Div

Vertical Position (Div)

5 V

0

Timebase

Time/Div

5 ms

Trigger

Type

Immediate

Source

Slope

Level (V)

0

Horizontal Position (%)

50

Instrument Control

Device

Simulate NI ELVIS II

Run

Stop

Autoscale

Acquisition Mode

Run Continuously

Print

Log