

1.) How can you make the current flowing through an IR LED increase linearly with voltage?

(B.) Add a resistor in Series.

2.) The photo transistor has only 2 legs since the base is an optical sensor, when the bjt's had 3 legs.

$$3.) A = A_c(1 + K_2 V_{in})$$

$$A = 10(1 + (0.1)(5)) = 10(1 + 0.5) = 10(1.5)$$

$$A = 15$$