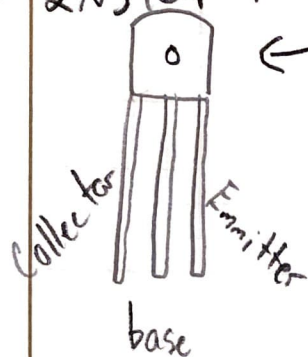


1.)

2N3904 Fet



Flat side on bottom

2.) See attached


3.) Operates as closed switch when it is in saturation region. It is in cutoff when it is open switch.

Because in saturation V_{CE} is small,
and in cutoff $i_C = 0$.




DC Sweep

Prelab #7 DC Transfer Characteristic

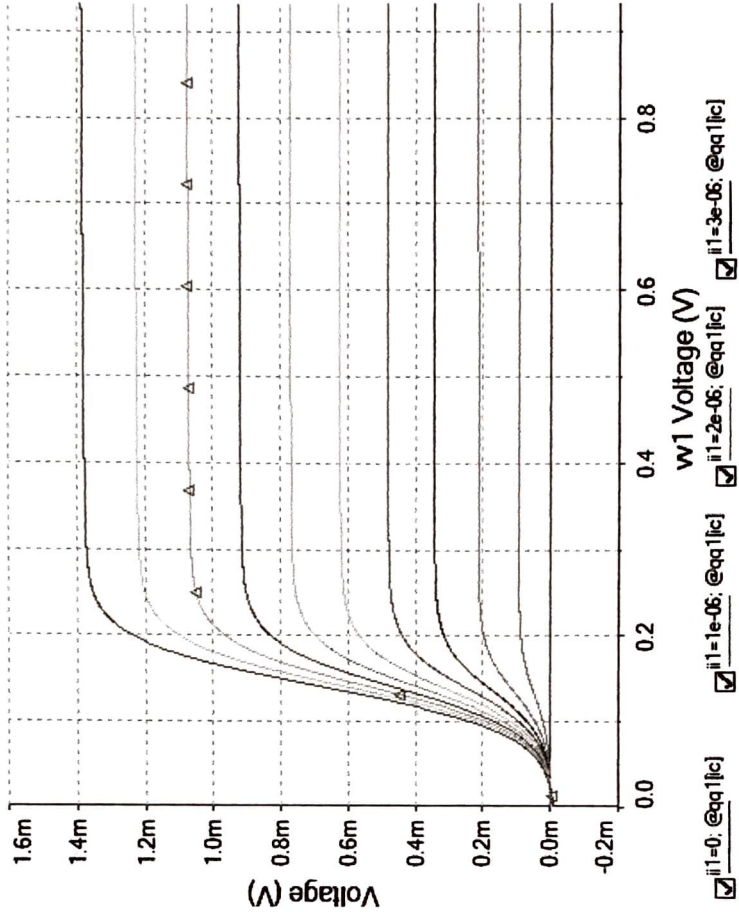

Selected Trace: $i1 = 8e-06$; @qq1[ic]

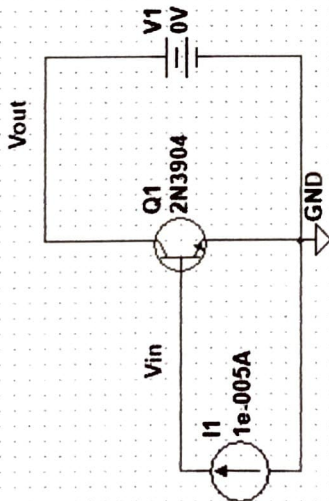

Gabriel Emerson