

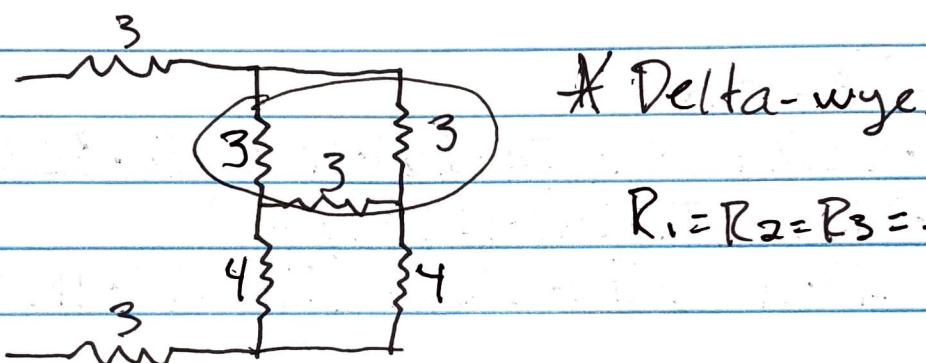


# Final Exam

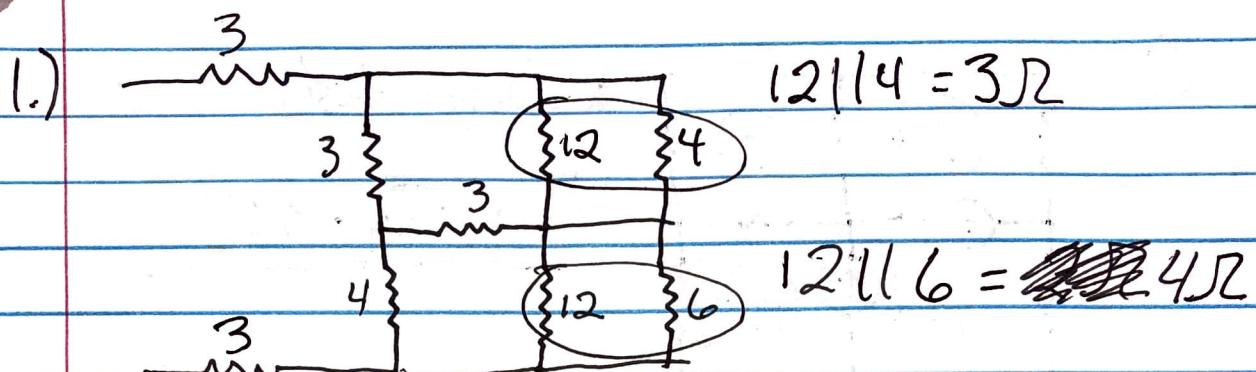

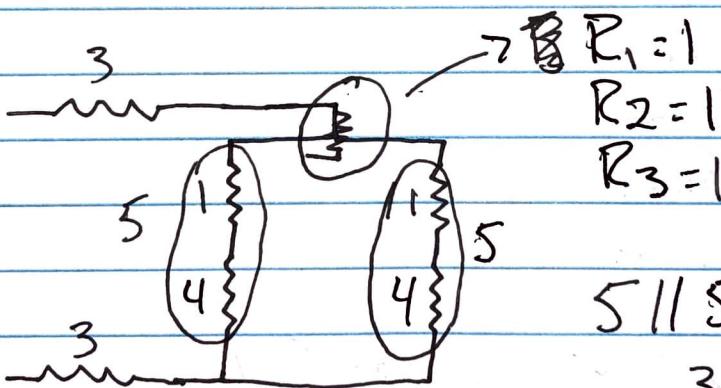
$$R_1 = R_2 = R_3 = \frac{3 \cdot 3}{3 + 3 + 3}$$



$$5 \parallel 5 = 2.5\Omega$$

$$2.5 + R_1 = 3.5\Omega$$

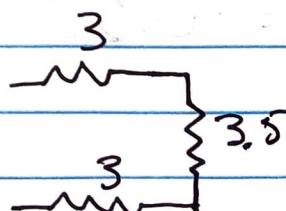


$$\Rightarrow 3 + 3.5 + 3 = 9.5\Omega$$

$$R_{eq} = 9.5\Omega$$

$$P_{sup} = I^2 \cdot R_{eq} = 5^2 \cdot 9.5 = \underline{\underline{237.5W}}$$

2.)

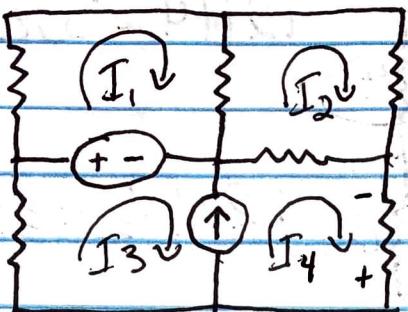

\* Super Mesh.

$$V_0 = -I_4 \cdot 3k\Omega$$

$$I_4 - I_3 = 4mA$$

$$I_3 \cdot 6k\Omega + 18 + (I_4 - I_2) \cdot 1k\Omega + I_4 \cdot 3k\Omega = 0$$

$$I_1 \cdot 3k\Omega + (I_1 - I_2) \cdot 1k\Omega - 18 = 0$$

$$(I_2 - I_1) \cdot 1k\Omega + I_2 \cdot 6k\Omega + (I_2 - I_4) \cdot 1k\Omega = 0$$

$$I_1 = 4.667mA$$

$$I_2 = 0.667mA$$


$$I_3 = -3.33mA$$

$$I_4 = 0.667mA$$

$$V_0 = -0.667 \cdot 3k\Omega = \underline{\underline{-2V}}$$


# Final Exam.

3.)

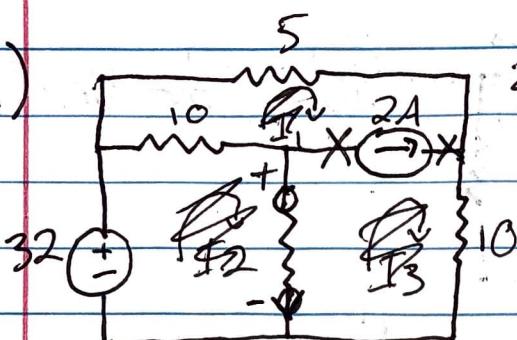

~~$$F_{\text{sum}} = 32 + 5I_1 = 10 \cdot I_1 \Rightarrow I_1 = 12.2A$$~~

Solve for  $I_N$


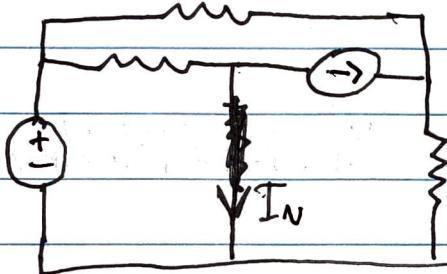


$$\begin{aligned} I_1 &= 3.8 \\ I_2 &= 4 \\ I_3 &= 2.8 \end{aligned}$$

$$I_N = I_2 - I_3 = 4 - 2.8 = \underline{1.2A}$$

$$R_N = 10\Omega$$


Norton Circuit.

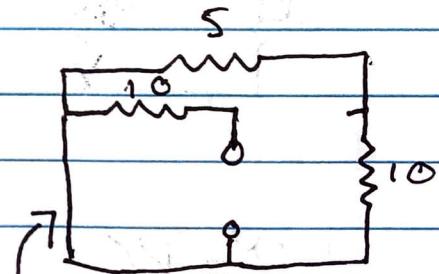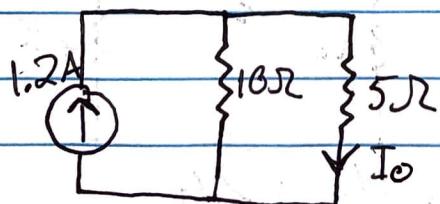

The 5Ω  
Are shorted by


$$I_O = 1.2 \cdot \frac{10}{5+10} = \underline{0.8A}$$

4.)

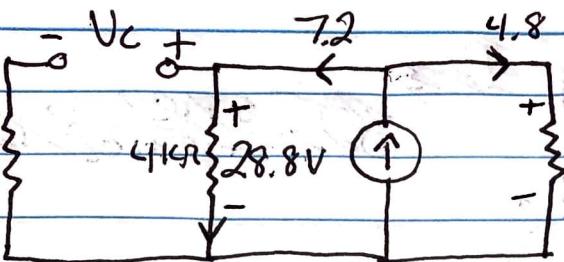
Solve for  $U_C$ .

$$12mA \cdot \frac{6}{4+6} = 7.2$$

$$U_C = 28.8V$$

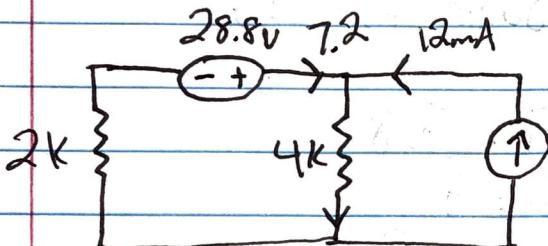

$$K_1 + K_2 = 19.2mA$$

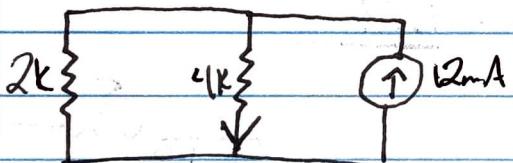

$$K_1 = 12 \cdot \frac{2}{4+2} = 4mA$$


$$K_2 = 19.2 - 4 = 15.2$$

$$\gamma = RC$$

$$C = 1.667\mu F$$

$$R = 4.4k\Omega$$

$$\Rightarrow \gamma = 7.3348$$

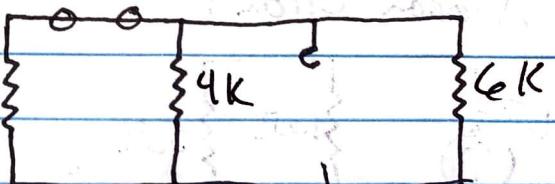


$$4 \parallel 6 = 2.4$$

$$2.4 + 2 = 4.4k = R$$

$$\Rightarrow 4 + 15.2e^{-t/7.3348} mA$$

# Final Exam

5.)

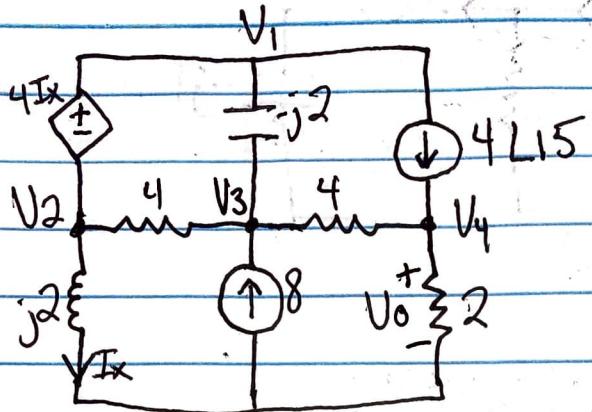

$$V_0 = V_4$$

~~Equations~~

$$1 \quad V_1 - V_2 = 4I_x$$

$$2 \quad \frac{V_1 - V_3}{-j2} + 4L15 + \frac{V_2 - V_3}{4} + \frac{V_2}{j2} = 0$$

$$3 \quad \frac{V_3 - V_1}{-j2} + \frac{V_3 - V_2}{4} + \frac{V_3 - V_4}{4} - 8 = 0$$

$$4 \quad -4L15 + \frac{V_4 - V_3}{4} + \frac{V_4}{2} = 0$$

$$5 \quad I_x = \frac{V_2}{j2}$$

$$V_1 =$$

$$V_2 =$$


$$V_3 =$$

$$V_4 =$$


$$I_x =$$

$$V_0 = V_4 =$$
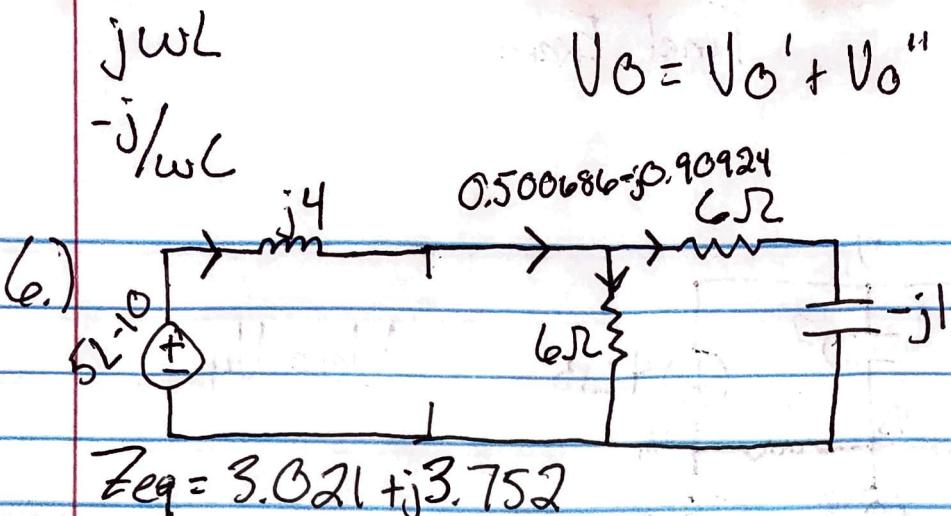
# Honestly, I put these equations in my TI-NSpire and a "Calculating" symbol came up for 10 minutes. I think I broke it! LOL.



$$V_O' = 3.14599 \angle -65.8587^\circ$$

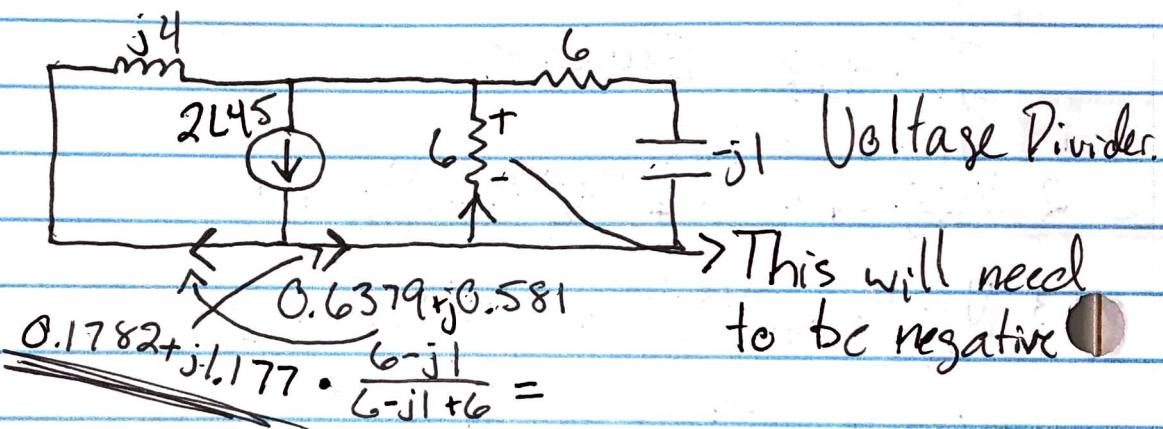

$$V_O'' = 3.51416 \angle 87.7421^\circ$$

$V_O = V_O' + V_O'' = 1.56247 \angle 24.2039^\circ$

# Final Exam

7.)  $Z_L = \text{complex Conjugate of } Z_{th}$


$$Z_{th} = \text{parallel } = 0.5 + j0.5$$

$$Z_{th} = 1 + (0.5 - j0.5) \Rightarrow 1.5 - j0.5$$

$$\boxed{Z_L = 1.5 + j0.5}$$

$$V_{th} = 5 \text{ V}$$

Thevenin Circuit

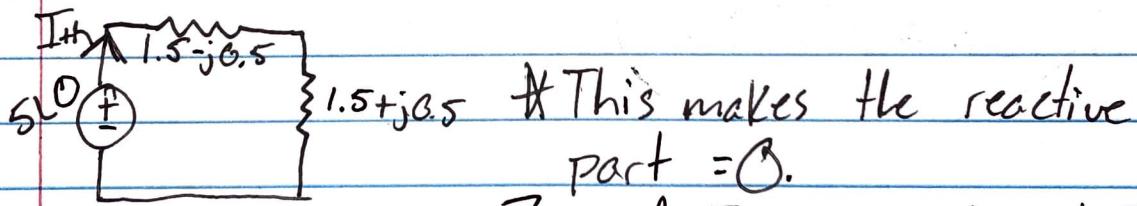

$$Z_{eq} \text{ of Thevenin's} = 1.5 + 1.5 = 3 \Omega$$


$$I_{th} = \frac{5}{3} = 1.667 \text{ A}$$

$$I_{th} \cdot 1.5 + j0.5 = V_L$$

$$I_{th} \cdot V_L = P_{L,\max} = 4.1675 + j1.38917$$

$$\boxed{4.3929 + j18.4349}$$

8.)

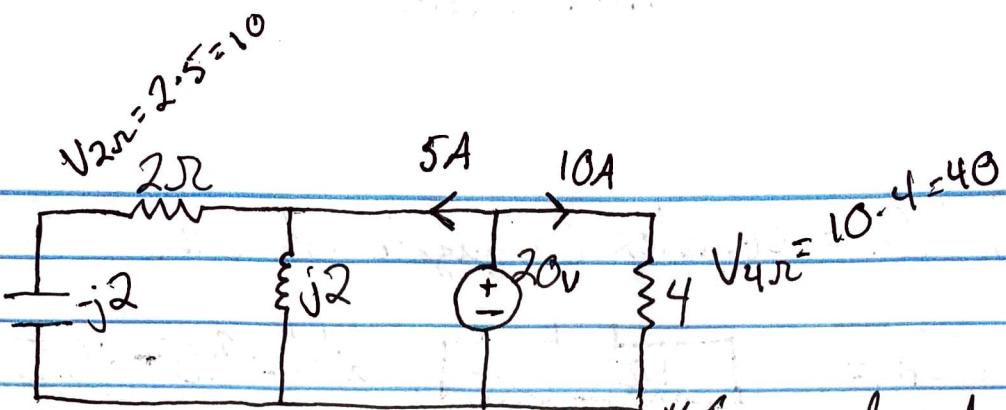

$$Z_{eq} = \frac{4}{3} \text{ or } 1.33$$

$$I_s = \frac{20}{1.33} = 15A$$

$$S_{vs} = 20 \cdot 15A = -300W \quad * \text{ Since it says absorbed.}$$

\* Caps and inductors absorb NO real power.

$$S_{4R} = 400W$$

$$S_{j2R} = 0$$


$$S_{2R} = 50W$$

$$S_{j2R} = 0$$

$$S_{vs} = -300W$$

# Final Exam.

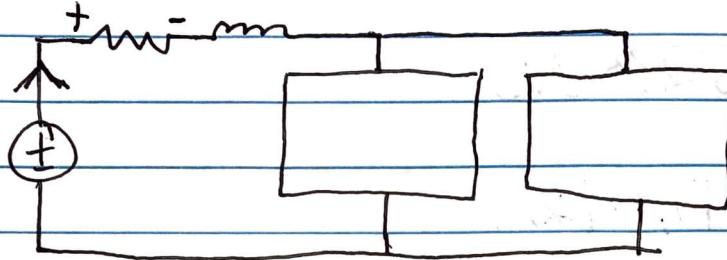9.)  $P_{load} = U_{load} \cdot I_{load} \cdot \text{pf}$



$$130\text{ kW} = 480 \cdot I \cdot \text{pf}$$

$$I = 231.481$$

$$150\text{ k} = 480 \cdot I \cdot \text{pf}$$

$$I = 325.521$$

$$U = 325.521 \cdot 0.4\Omega$$

$$U_S = 130.208\text{ V}$$

#60Hz 377t

10.)  $Q_{\text{old}} = P \tan(\cos^{-1}(\rho_f))$

$Q_{\text{old}} = 52350.3$

$Q_{\text{new}} = 17,092.7$

$$Q_{\text{old}} - Q_{\text{new}} = \omega \cdot V_{\text{rms}}^2 \cdot C$$

$$35257.6 = 377 \cdot 220^2 \cdot C$$

$$\underline{C = 0.001932}$$

or  
1.932 mF

Bonus: Larger, since the component of capacitors are negative  $j$ , we need  $\rho_f$  to be negative (since leading is negative) we need a higher capacitor value.