

1.) NMOS

$$K_P = 300 \frac{\text{mA}}{\text{V}^2}$$

$$V_{TO} = 0.5\text{V}$$

$$V_{DD} = 3\text{V}$$

PMOS

$$K_P = 150 \frac{\text{mA}}{\text{V}^2}$$

$$V_{TO} = -0.5\text{V}$$

0.25  $\mu\text{m}$  CMOS

$$\frac{W_P}{L_P} = \frac{300}{150} \cdot 2 = \frac{4}{1}$$

NMOS	PMOS
$W = 0.5 \mu\text{m}$	$W = 1 \mu\text{m}$
$L = 0.25 \mu\text{m}$	$L = 0.25 \mu\text{m}$

2.) For CMOS:

a.)  $V_L = 0\text{V}$      $V_H = 3\text{V}$

b.) Standby power consumption = 0V

c.)  $V_L$  and  $V_H$  will be the same.

d.)  $V_{DD} \rightarrow 4\text{V}$  : Standby power consumption = 0V

e.)  $V_{IL} = 1.25\text{V}$      $V_{IH} = 1.75\text{V}$

$$V_{OH} = 2.75\text{V}$$

$$V_{OL} = 0.25\text{V}$$

f.) Noise Margin Low  $\rightarrow 1$



Noise Margin High  $\rightarrow 1$

g.) Symmetry remains but it is shifted to 2V due to  $V_{DD}$  being 4V. The circuit does still work like an inverter. However the NML and NMH will increase which is something we do not want.



3a)  $V_{in} = 1V, V_{in} = 2V$

1V  $\begin{cases} \frac{1}{2}(300)(2)(1-0.5)^2 = 75mA \rightarrow I_{DS}, NMOS \\ I_{SD} = \frac{1}{2}(150)(4)(-2-(-0.5))^2 = 675mA, PMOS \end{cases}$

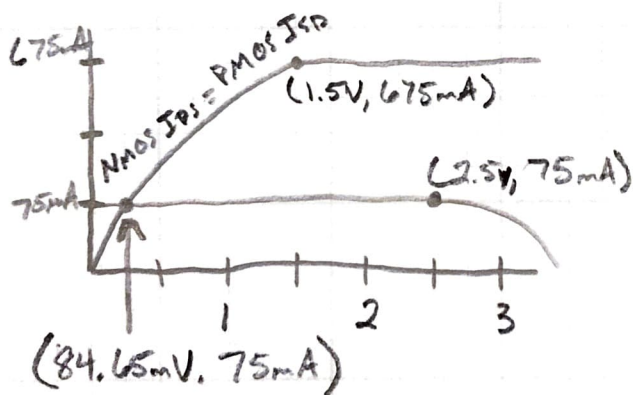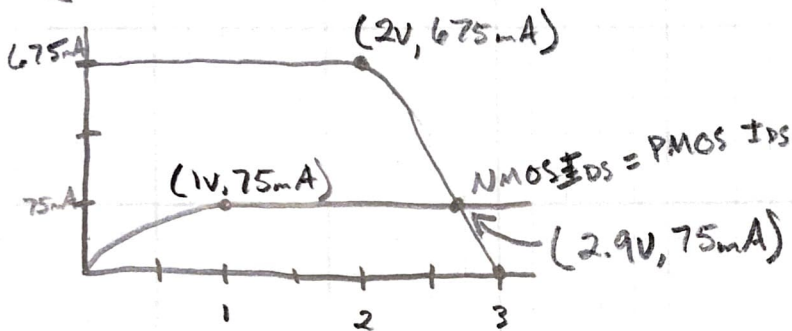2V  $\begin{cases} I_{DS sat} = \frac{1}{2}(300)(2)(2-0.5)^2 = 675mA, NMOS \\ I_{DS sat} = \frac{1}{2}(150)(4)(-1-(-0.5))^2 = 75mA, PMOS \end{cases}$



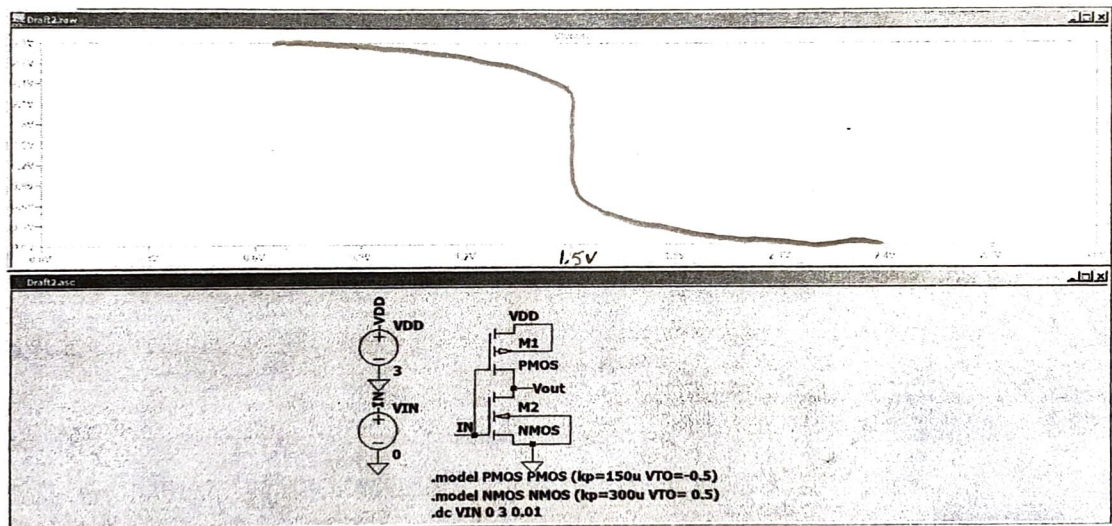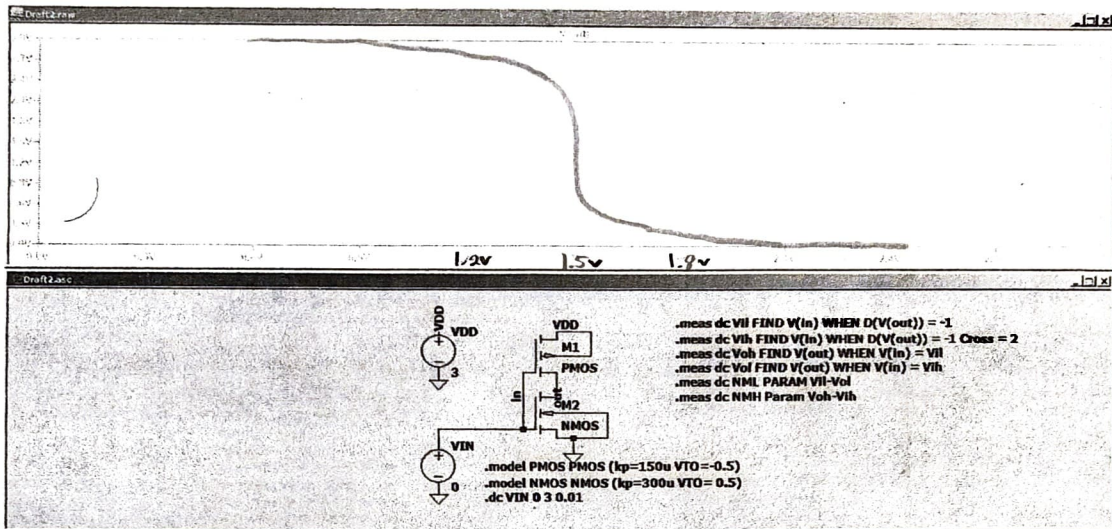yes hand calculations are close to simulations.







Instance "M2": Length shorter than recommended for a level 1 MOSFET.  
 Instance "M2": Width narrower than recommended for a level 1 MOSFET.  
 Instance "M1": Length shorter than recommended for a level 1 MOSFET.  
 Instance "M1": Width narrower than recommended for a level 1 MOSFET.

vil: v(in)=1.24998 at 1.24998  
 vih: v(in)=1.75002 at 1.75002  
 voh: v(out)=2.75002 at 1.24998  
 vol: v(out)=0.24998 at 1.75002  
 nml: vil-vol=0.999999  
 nmh: voh-vih=1

Date: Thu Feb 28 11:38:56 2019  
 Total elapsed time: 0.102 seconds.

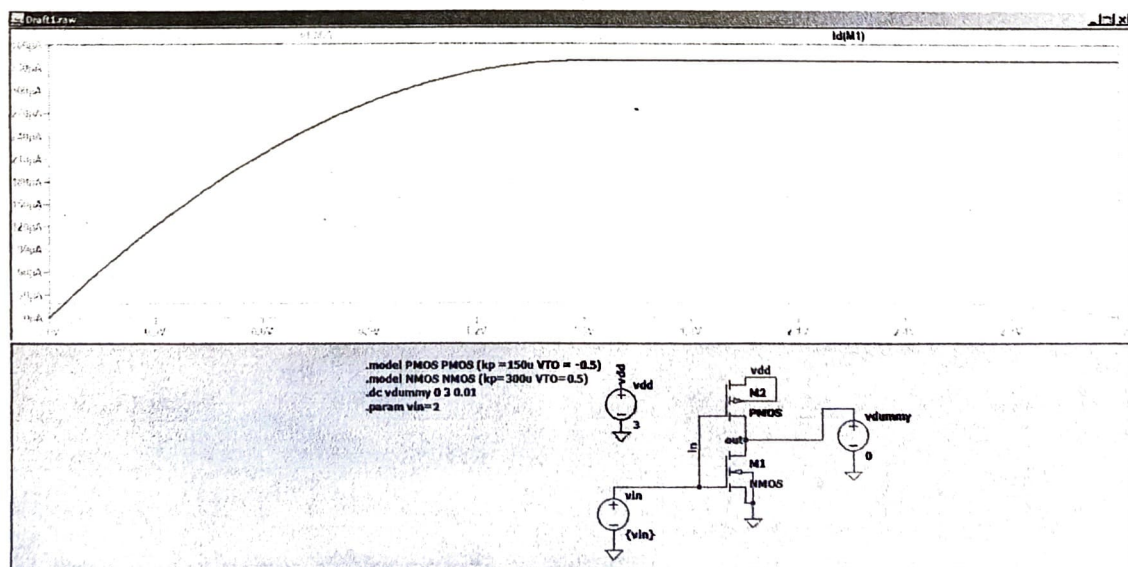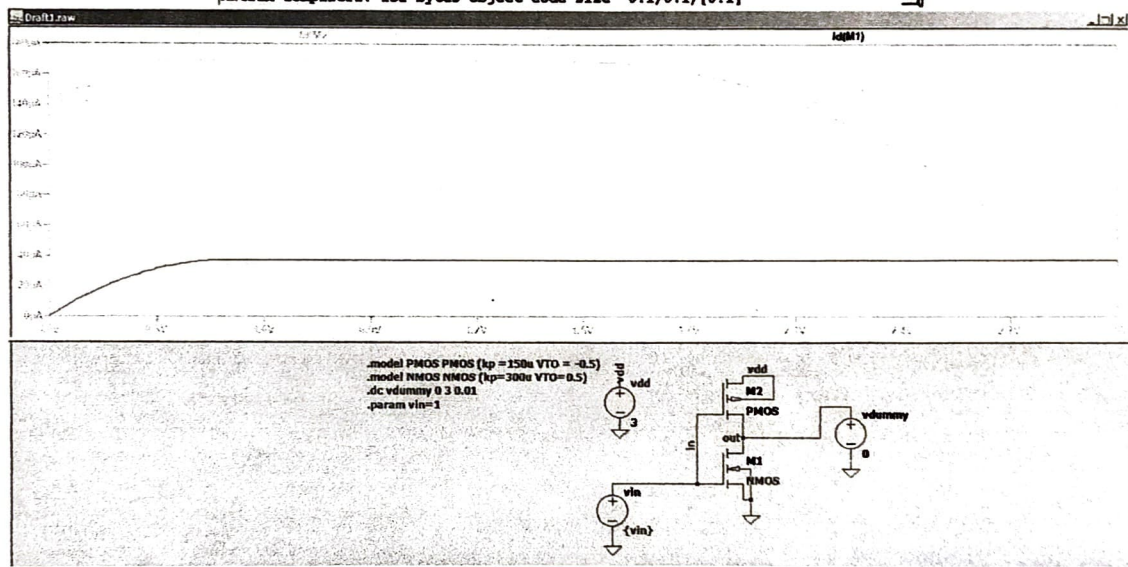tnom = 27  
 temp = 27  
 method = trap  
 totiter = 637  
 traniter = 0  
 tranpoints = 0  
 accept = 0  
 rejected = 0  
 matrix size = 3  
 fillins = 0  
 solver = Normal  
 Matrix Compiler1: 132 bytes object code size 0.1/0.1/[0.1]



i=1.430W y=56.94uA