

ELEC 2110

Electric Circuit Analysis

Gabriel Emerson

Jake Bryson

September 17, 2019

Section 002


Recitation & MultiSim: Thevenin's and Norton's Theorem

Introduction

The student will work to solve problems related to Thevenin's and Norton's Theorem. Given circuits, solve using Thevenin's and Norton's Theorem, then verify using Multisim.

Exercise 1

Use Thevenin's theorem to find V_o and use MultiSim to verify the answer.

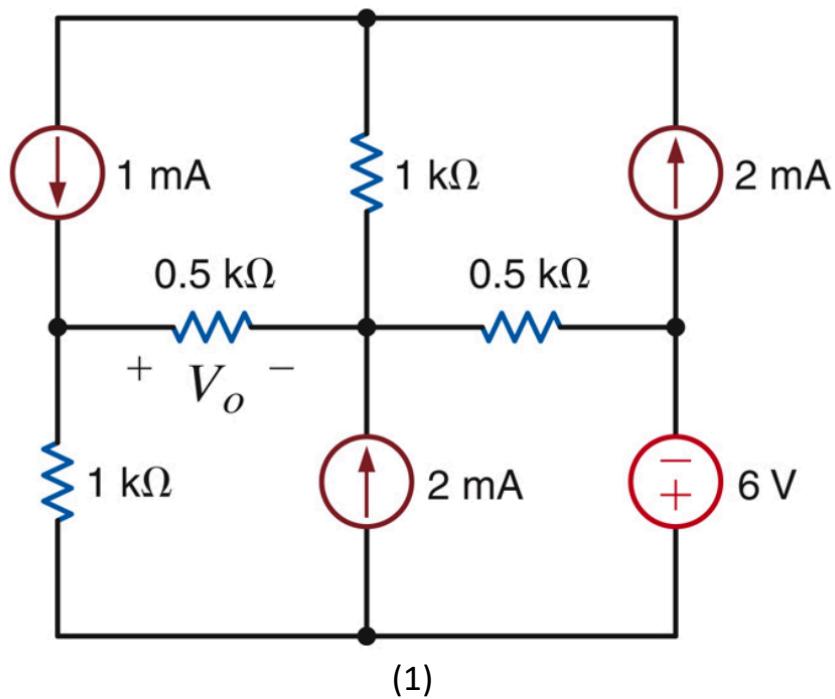

Circuit 1


$$V_{Th} = 1K(1_m) - 0.5K(3.) + 6 \Rightarrow 5.5V$$
$$R_{Th} = 1.0K + 0.5K = 1.5k\Omega$$

Equations for exercise 1 circuit 1

(2)


Summary Table

V _{th}	5.5V
R _{th}	1.5k Ohm
V _o	1.375V

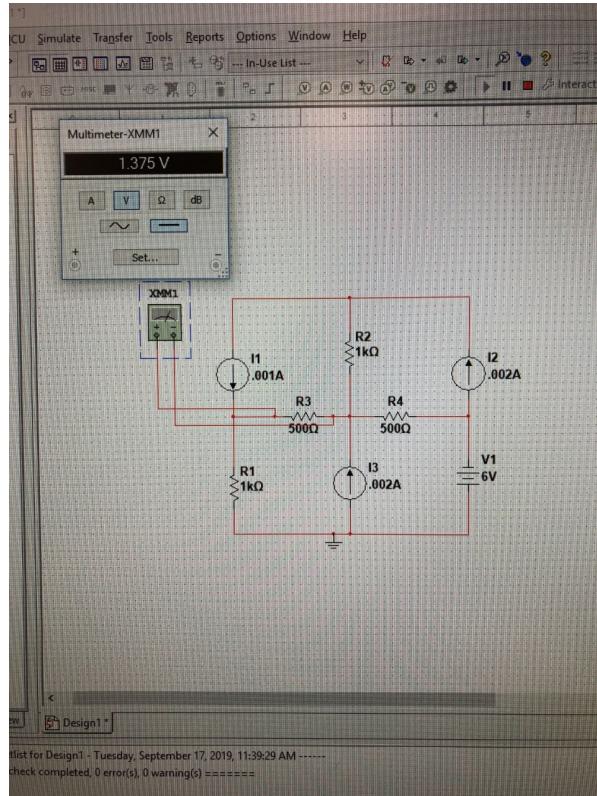

(3)

Verify Vo

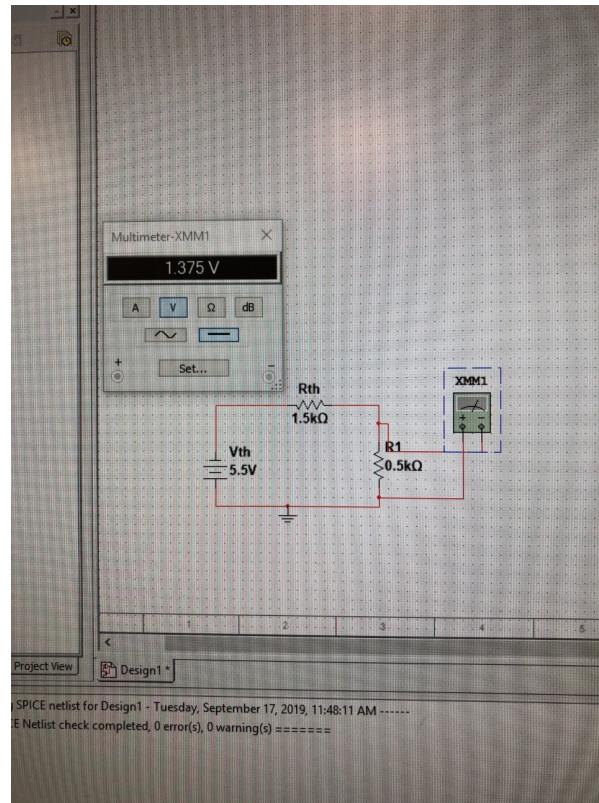


(4)

Verify using Thevenin's Circuit

Exercise 2

Given a new circuit, find R_L and use it to find maximum Power (P_{max}) for R_L . Then plot R_L and P_{max} .

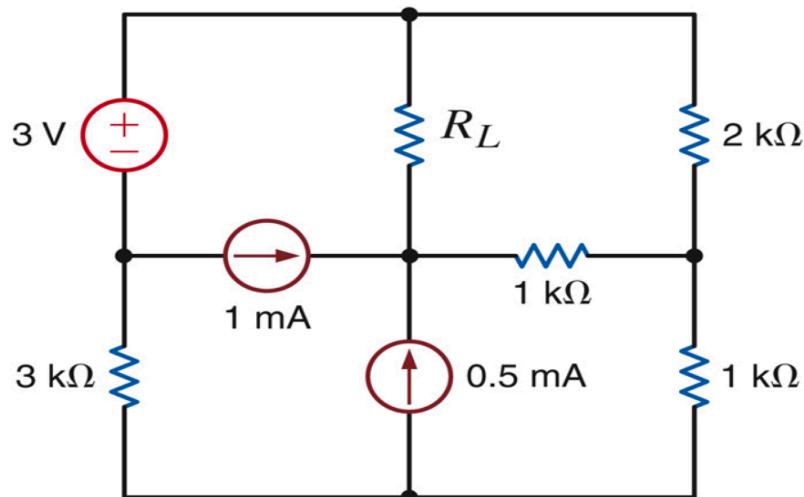

Circuit 2

(5)

#2 $V_1 - V_2 = 3V$

$$\frac{(V_1 - V_4)}{2k} + \frac{V_2}{3k} = -1mA$$

$$\frac{V_3 - V_4}{1k} = 1.5mA$$

$$\frac{V_4 - V_1}{2k} + \frac{V_4 - V_3}{1k} + \frac{V_4}{1k} = 0$$

$$V_1 = 0.75$$

$$V_2 = -2.25$$

$$V_3 = 2.75$$

$$V_4 = 1.25$$

$$V_{th} = 0.75V$$

$$R_{th} = (2k || 1k + 3k) + 1k$$

$$= 2.33k$$

$$V_{RL}/R_{th} = 1/2.33k$$


$$= 429.18mW$$

(6)

Equations for exercise 2 circuit 2


Summary Table

V1	0.75V
V2	-2.25V
V3	2.75V
V4	1.25V
Vth	2.00V
Rth	2.33k Ohm
V _{RL} /R _{th} = P _{max}	= 1/(2.33k) = 429.18mW

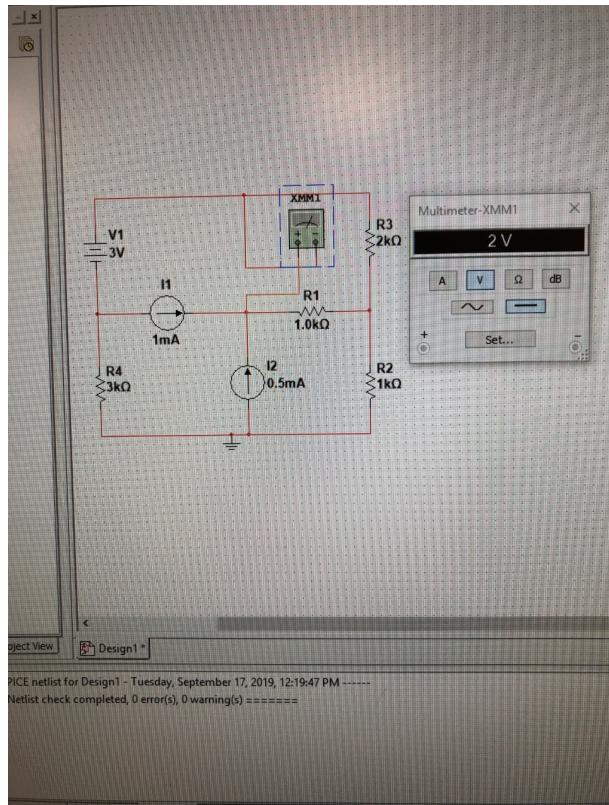


(7)

Verify V_{th}

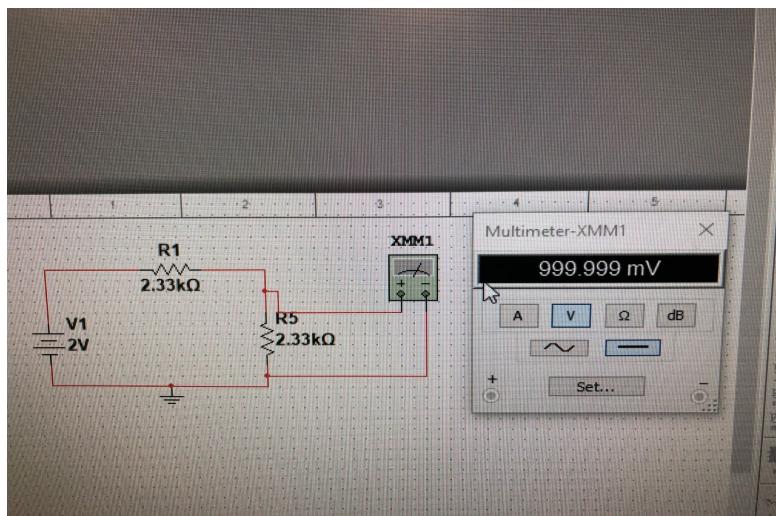

(8)

Verify using Thevenin's Circuit

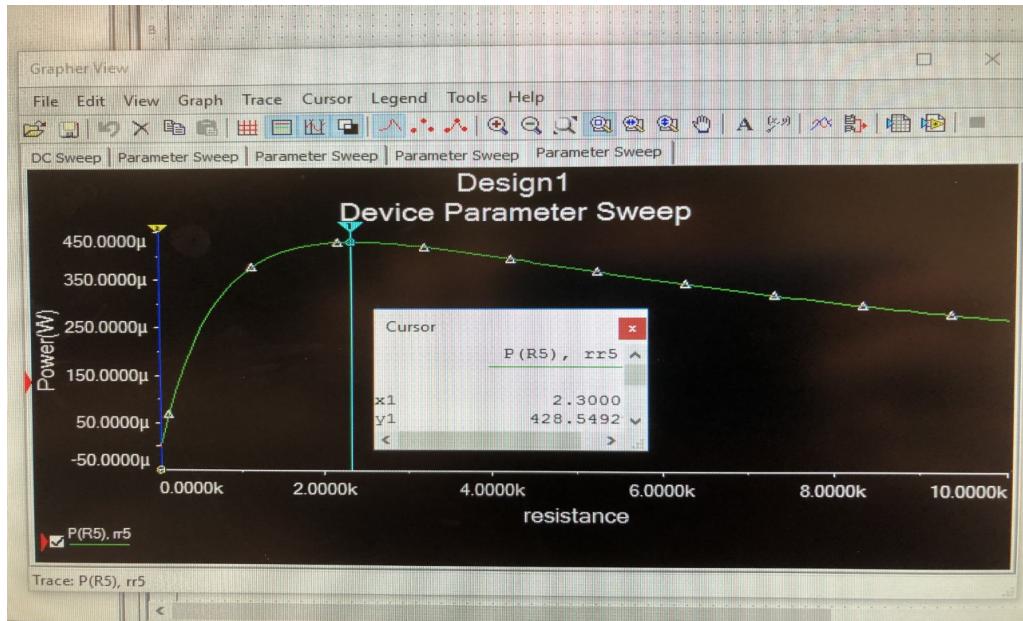


(9)

Parameter sweep for exercise 2 (very sorry it is black)

Exercise 3

Use Thevenin's Theorem to solve for V_x in circuit 3. Use MultiSim to verify the answer.

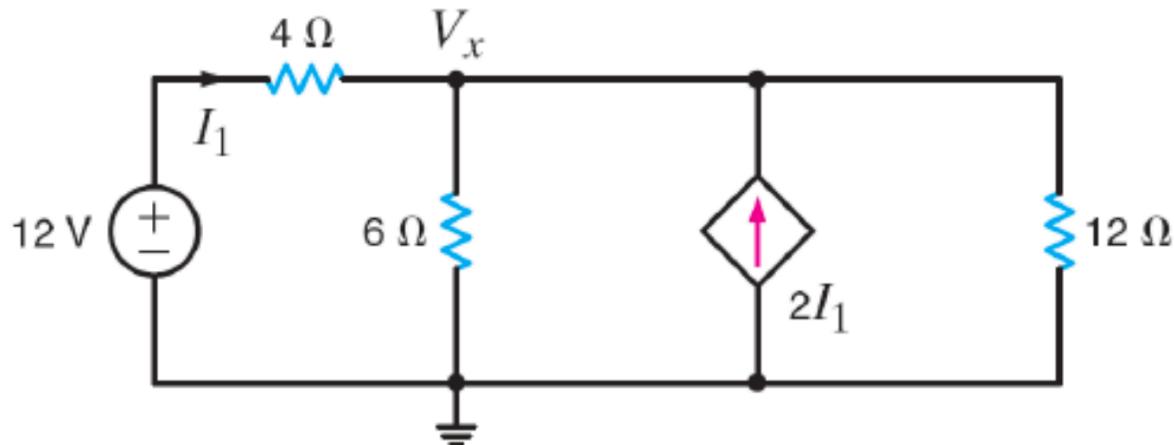

Circuit 3

(10)

Lab 5

$$\frac{V_{oc} - 12}{4\Omega} + \frac{V_{oc}}{6} - 2I_1 = 0$$

$$I_1 = 12V - V_{oc}$$

$$V_{oc} = 9.818V$$

$$4\Omega \Rightarrow 1.091mA$$

$$4I_1 + 6(I_1 - I_2) = 12$$

$$6(I_1 - I_2) = 0$$

$$I_3 - I_2 - 2I_1 = 0$$

$$I_1 = I_2 = 3A$$

$$I_3 = I_{sc} = 9A$$


$$R_{TH} = \frac{9.818}{9A} \leftarrow R_{TH}$$

(11)

Equations for Exercise 3 Circuit 3


Summary Table

V _{oc}	9.818V
I _{sc}	9A
R _{th} = V _{oc} /I _{sc}	= 9.818/9 = 1.091 Ohms

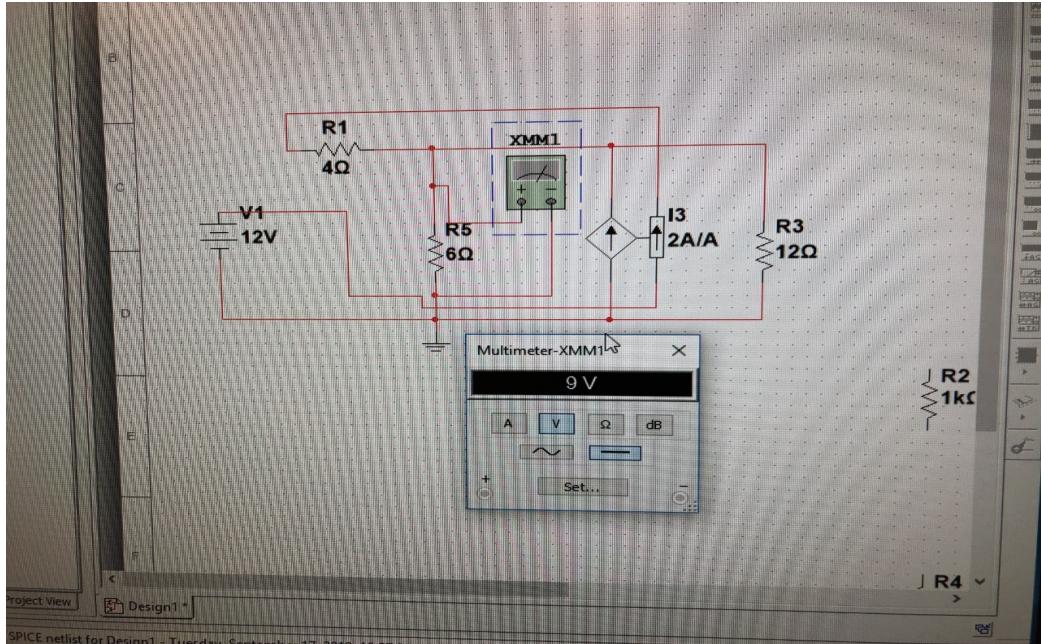

(12)

Verify V_x

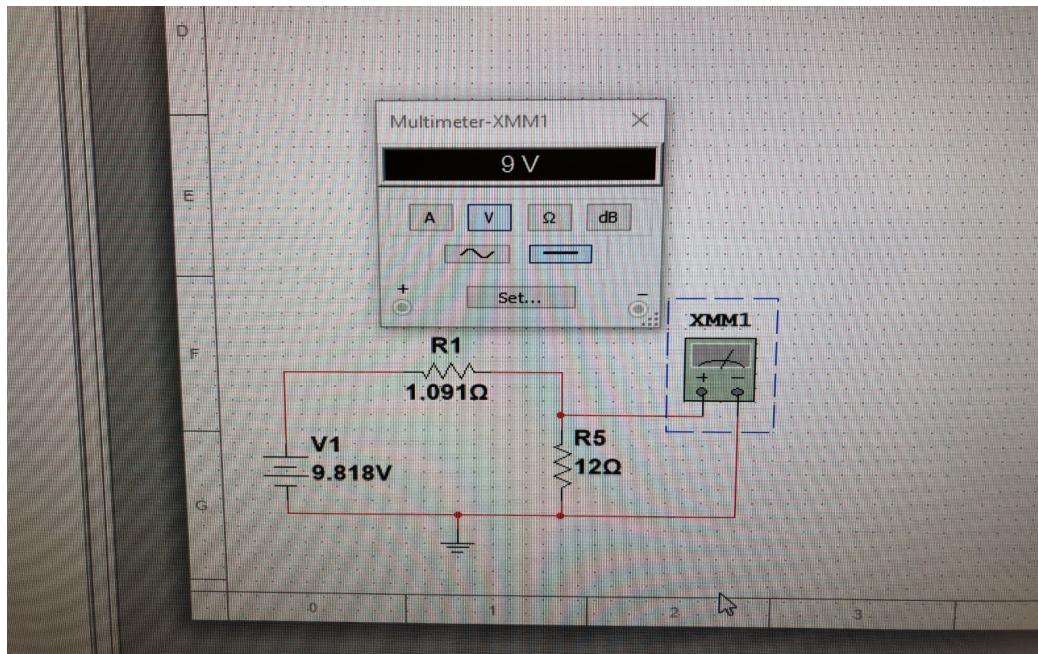


(13)

Verify using Thevenin's Circuit

Exercise 4

Build the Thevenin circuit between nodes A and B for the given circuit. Then build it in MultiSim and verify your answer using the Ohmmeter.

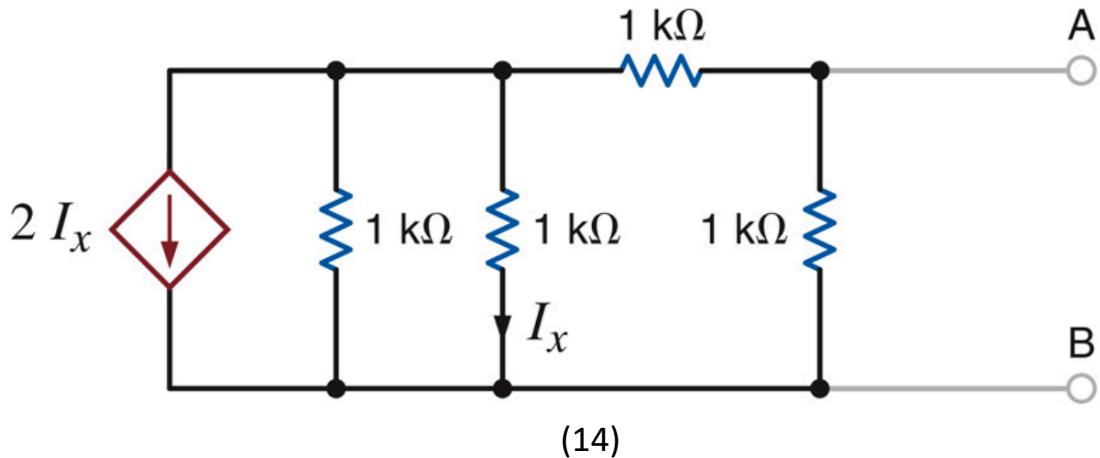

Circuit 4

$2\left(\frac{V_x}{1k}\right) + \frac{V_x}{1k} + \frac{V_x}{1k} + \frac{V_x - V_{ab}}{1k} = 0$

 $V_x = 0.2V$

$I_{SC} = \frac{V_{ab} - V_x}{1k} + \frac{V_{ab}}{1k} = 18mA$


$R_{th} = \frac{1V}{1.8mA} = 555.5\Omega$

(15)

Equations for Exercise 4 Circuit 4


Summary Table

Vx	0.2V
Isc	1.8mA
Rth	555.5 Ohm

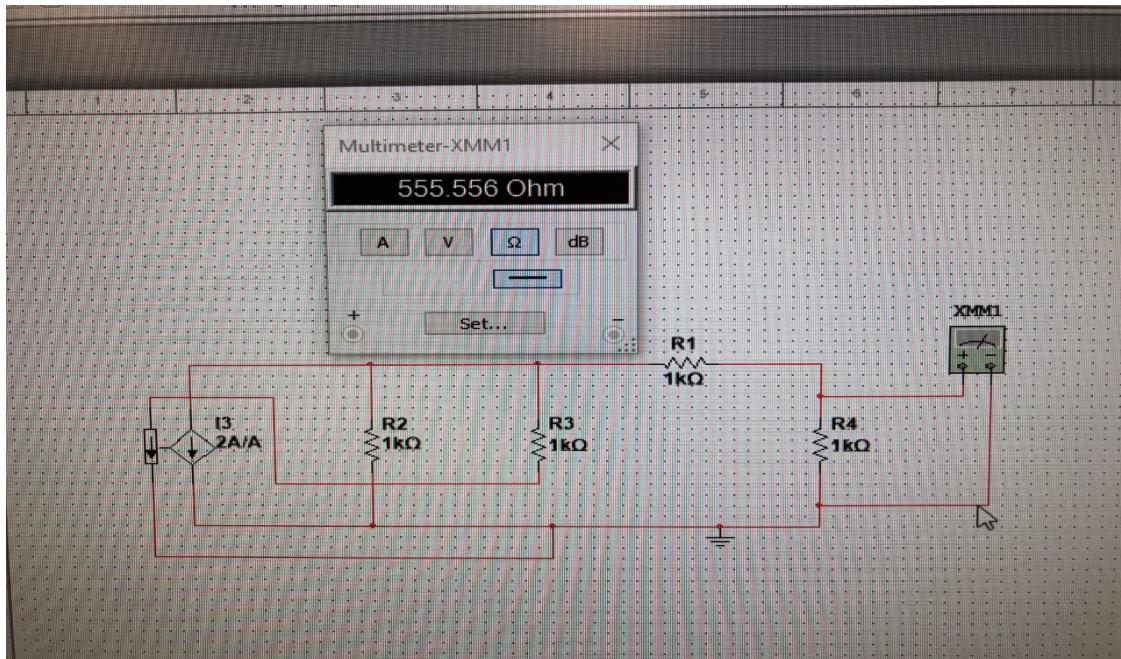

(16)

Verify Rth

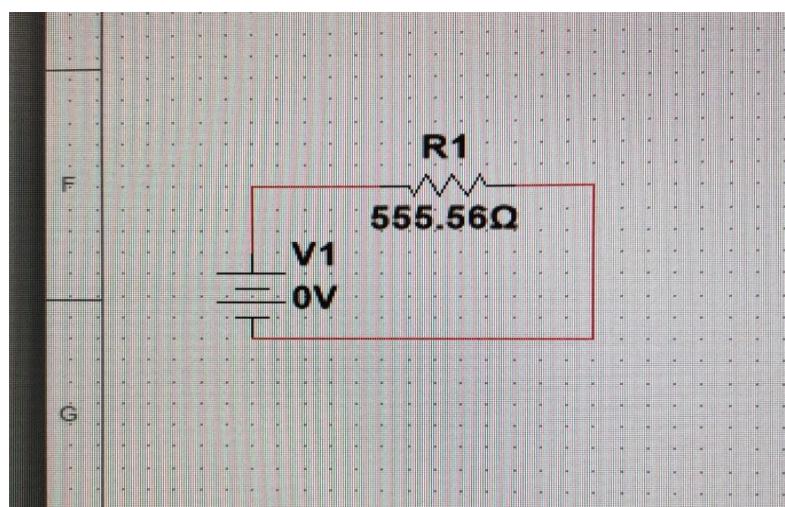


(17)

Verify using Thevenin Circuit

Exercise 5

Given a new circuit, find R_L and P_{max} , and verify using MultiSim. Then plot resistance (R_L) / Power (P_{max}).

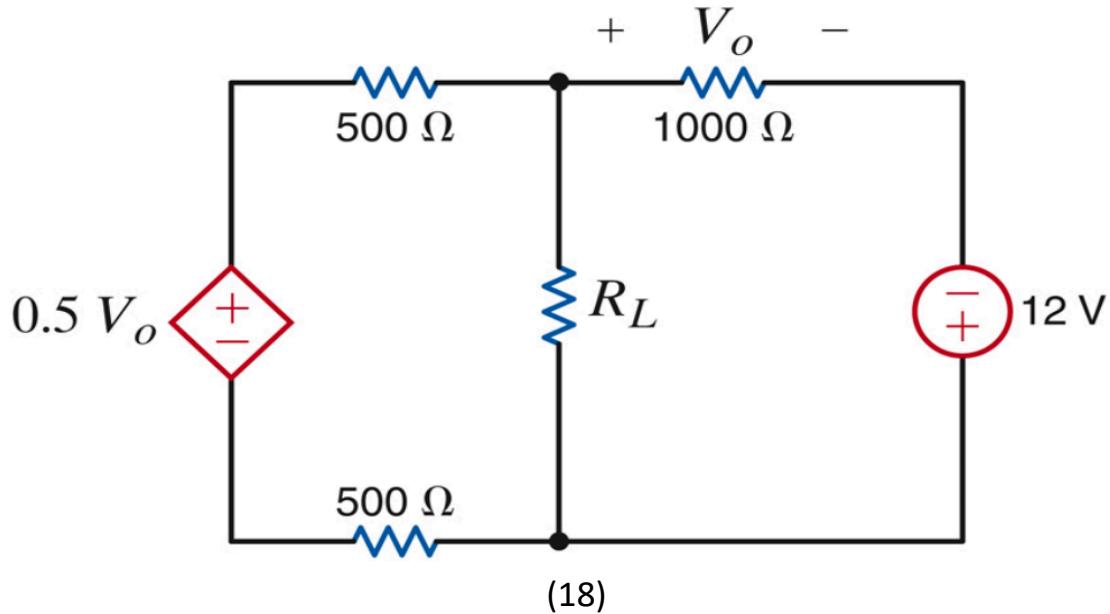

Circuit 5

$\#5. \quad V_o = I(1k)$ $I(500 + 1k + 500) - 0.5(I \cdot 1k) = 12$ $I = 8mA$ $V_{th} = 12 - V_o = 4V$ $R_{th} = 4V / 8mA = 666.67$	$\frac{V_{RL}}{R_{th}} = 6mW$
---	-------------------------------


$I_2 \cdot 1k = 12mA$ $I_1(1000) - 0.5(I_2 \cdot 1k) = 0$ $I_1 = 6mA$ $I_o = 6mA$	
--	--

(19)

Equations for Exercise 5 Circuit 5


Summary Table

I	8mA
I ₁	6mA
I ₂	12mA
I _n	6mA
V _{th}	4V
R _{th}	666.67 Ohm
P _{max}	6mW

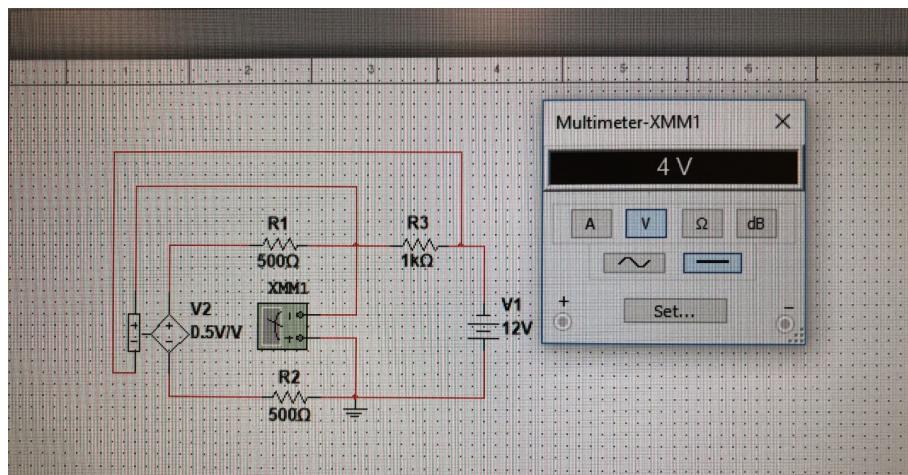


(20)

Verify V_{th}

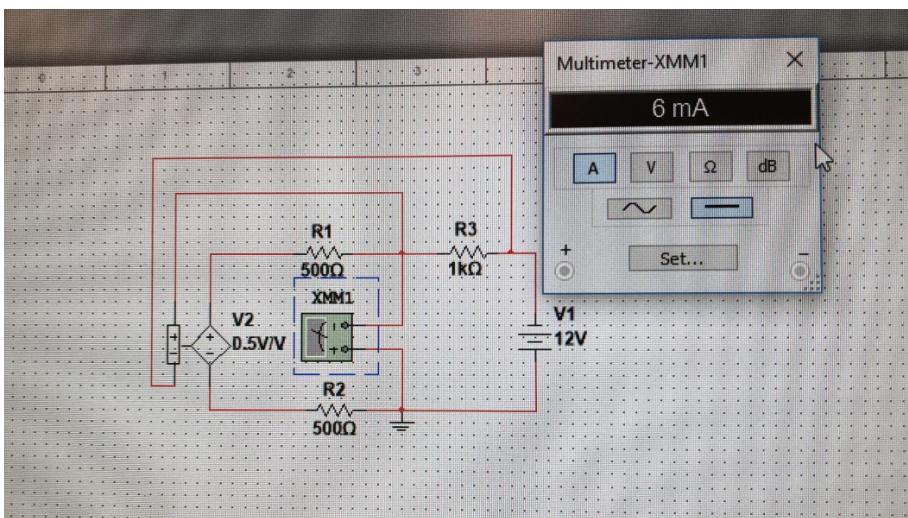


(21)

Verify Current

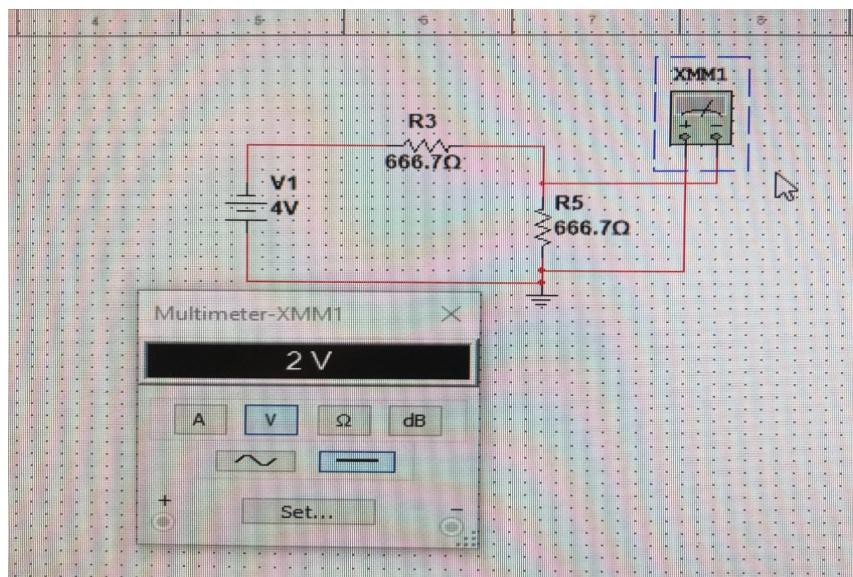

(22)

Verify V across Rth

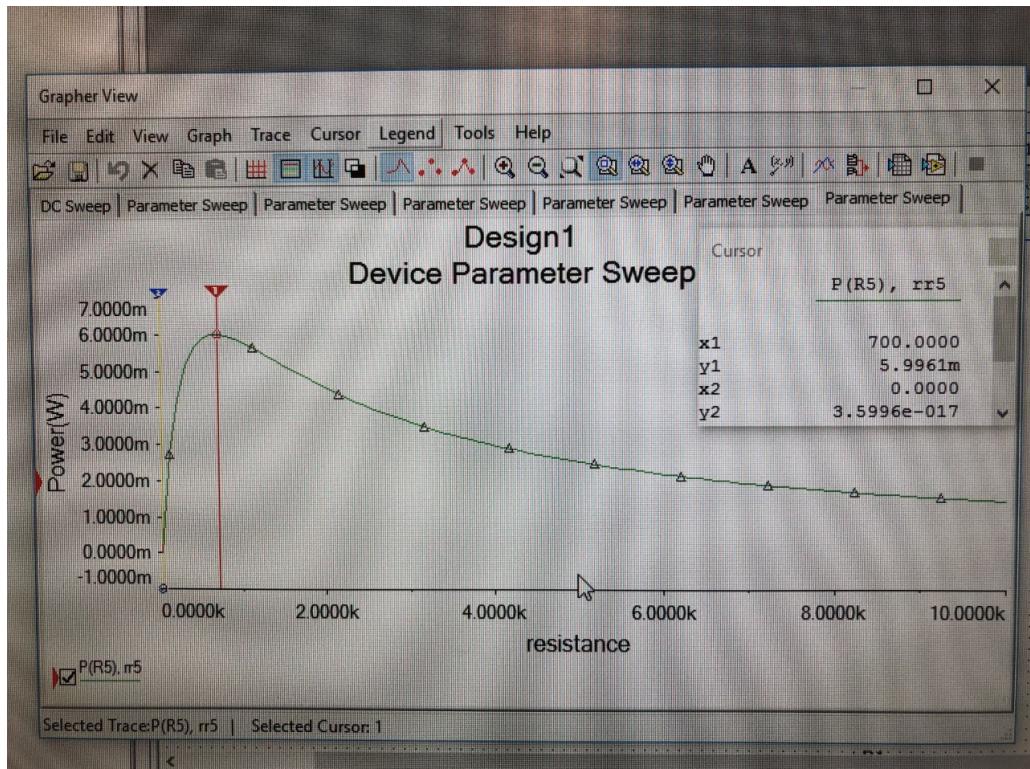

(23)

Parameter sweep for Exercise 5

Conclusion

Using Norton's and Thevenin's Theorem makes solving certain circuits much easier. Lab 5 is a crucial beginning for the student to understand there are many ways to solve circuits, and depending on the circuit, certain ways are easier than others. Thevenin's Circuits play a big role in Electrical Engineering and it is very important to understand its strengths and weaknesses.

Bibliography

1. Circuit 1 given for exercise 1
2. Hand-written equations for exercise 1, circuit 1
3. Verify V_o using MultiSim for exercise 1, circuit 1
4. Verify using Thevenin Circuit for exercise 1, circuit 1
5. Circuit 2 given for exercise 2
6. Hand-written equations for exercise 2, circuit 2
7. Verify V_{th} using MultiSim for exercise 2, circuit 2
8. Verify using Thevenin Circuit for exercise 2, circuit 2
9. Parameter sweep of Resistance and Power for exercise 2, circuit 2
10. Circuit 3 given for exercise 3
11. Hand-written equations for exercise 3, circuit 3
12. Verify V_x using MultiSim for exercise 3, circuit 3
13. Verify using Thevenin Circuit for exercise 3, circuit 3
14. Circuit 4 given for exercise 4
15. Hand-written equations for exercise 4, circuit 4
16. Verify R_{th} using MultiSim for exercise 4, circuit 4
17. Verify using Thevenin Circuit for exercise 4, circuit 4
18. Circuit 5 given for exercise 5
19. Hand-written equations for exercise 5, circuit 5
20. Verify V_{th} using MultiSim for exercise 5, circuit 5
21. Verify Current using MultiSim for exercise 5, circuit 5
22. Verify using Thevenin Circuit for exercise 5, circuit 5
23. Parameter sweep of Resistance and Power for exercise 5, circuit 5