

ELEC 2210 PRE-LAB COVER PAGE
Complete and attach this page to the front of your pre-lab.

Meeting # 9 Mosfets & CMOS inverters
Title of Lab Experiment

Student Name: Emerson Gabriel
Name (Last, First, MI)

Student Email: gte0002
AU 7-character username

GTA: Paul Atilola
Name of your GTA

Section you are enrolled in: (Circle One) 1 2 3 4 5 6 7 8

Date pre-lab submitted: (dd / mm / yy): 3/15/21


I hereby certify that this pre-lab work was performed and written by me exclusively.


Student signature

Date signed

P dissipation MAX: 500 mW

Mosfet acts as open switch in the cutoff region because current can't flow between drain and source.

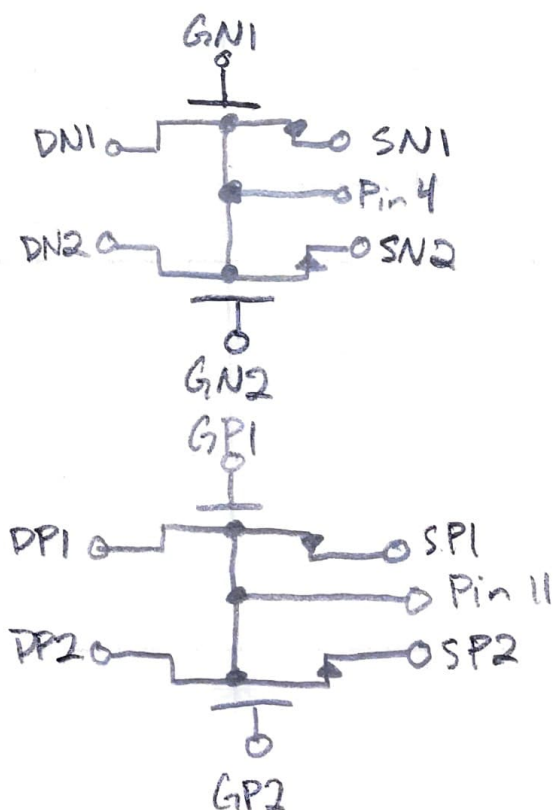
$$V_{C, \text{offset}} = 3.5 \text{ V}$$